

## Homework 4

Page 95, Chinese textbook

### Question 12

Considering a three-phase bridge fully-controlled rectifier circuit under a resistive load, if one thyristor cannot be conducted, what does the rectifier voltage waveform  $u_d$  look like? If one thyristor has been broken down and is a short circuit now, what is the influence on the other thyristors?

### Question 13

Considering a three-phase bridge fully-controlled rectifier circuit with  $U_2 = 100V$ , under a resistive and inductive load with  $R = 5\Omega$  and very large inductance, when  $\alpha = 60^\circ$ :

- 1) Draw the waveform of  $u_d$ ,  $i_d$  and  $i_{VT_1}$ ;
- 2) Calculate  $U_d$ ,  $I_d$ ,  $I_{dVT}$ , and  $I_{VT}$ .

### Question 15


Considering a three-phase half-wave controlled rectifier circuit connected to a EMF load with resistor and inductor, when  $U_2 = 100V$ ,  $R = 1\Omega$ ,  $L = \infty$ ,  $L_B = 1mH$ ,  $\alpha = 30^\circ$ ,  $E = 50V$ , calculate the value of  $U_d$ ,  $I_d$ ,  $\gamma$  and draw the waveform of  $u_d$ ,  $i_{VT_1}$ ,  $i_{VT_2}$ .

### Question 16

Considering a three-phase bridge uncontrolled rectifier circuit connected to a resistive and inductive load, with  $R = 2\Omega$ ,  $L = \infty$ ,  $U_2 = 100V$ ,  $X_B = 0.1\Omega$ , calculate the value of  $U_d$ ,  $I_d$ ,  $I_{VD}$ ,  $I_2$  and  $\gamma$ , and draw the waveform of  $u_d$ ,  $i_{VD}$ , and  $i_2$ .

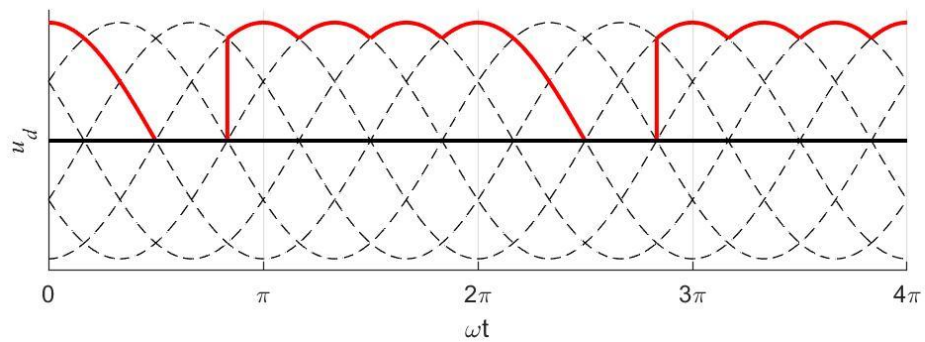**Answer 3.12**


Supposing the  $VT_1$  isn't turned on, the waveform of rectified voltage  $u_d$  is



If the  $VT_1$  is broken down to become short circuit and the thyristor  $VT_3$  and  $VT_5$  is turned on, power is shorted-circuited, which will make the  $VT_3$  and  $VT_5$  break down.

**Answer 3.13**

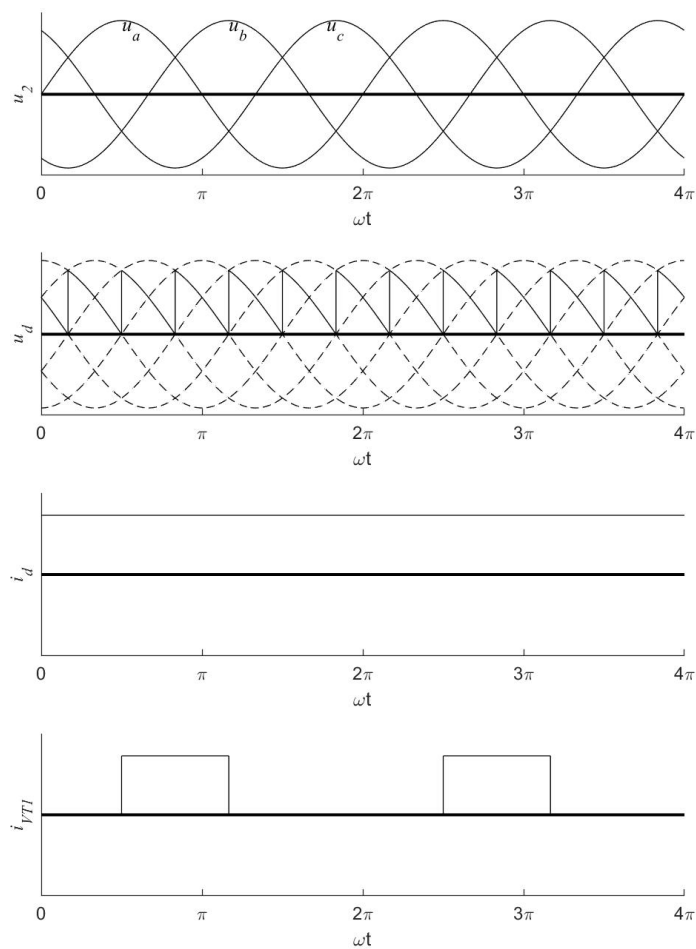(1) The waveform of  $u_d$ ,  $i_d$  and  $i_{VT1}$ :



(2) The result of  $U_d$ ,  $I_d$ ,  $I_{dVT}$ , and  $I_{VT}$ .

$$U_d = 2.34U_2 \cos \frac{\pi}{3} = 2.34 \times 100 \times \cos \frac{\pi}{3} V = 117V$$


$$I_d = \frac{U_d}{R} = \frac{117V}{5\Omega} = 23.4A$$

$$I_{DVT} = \frac{I_d}{3} = \frac{23.4A}{3} = 7.8A$$

$$I_{VT} = \frac{I_d}{\sqrt{3}} = \frac{23.4A}{\sqrt{3}} = 13.51A$$

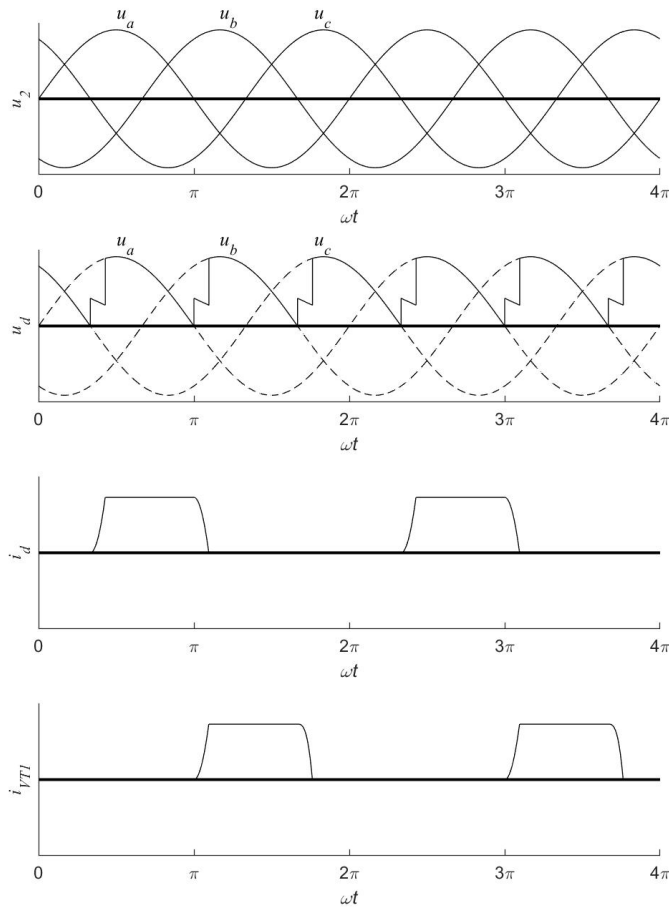**Answer 3.15**

the waveform of  $u_d$ ,  $i_{VT1}$ ,  $i_{VT2}$ :



Given that  $L_B = 1\text{mH}$ , it's known that

$$\begin{cases} U_d = 1.17U_2 \cos \alpha - \Delta U_d \\ \Delta U_d = \frac{3X_B I_d}{2\pi} \\ I_d = \frac{(U_d - E)}{R} \end{cases}$$

Solutions of equations are:

$$\begin{cases} U_d = 94.3V \\ \Delta U_d = 6.7V \\ I_d = 44.63A \end{cases}$$

We can get the relationship that


$$\begin{cases} \alpha = \frac{\pi}{6} \\ \gamma = 11.28^\circ \end{cases}$$

for the reason that

$$\cos \alpha - \cos(\alpha + \gamma) = \frac{2I_d X_B}{\sqrt{6}U_2}$$
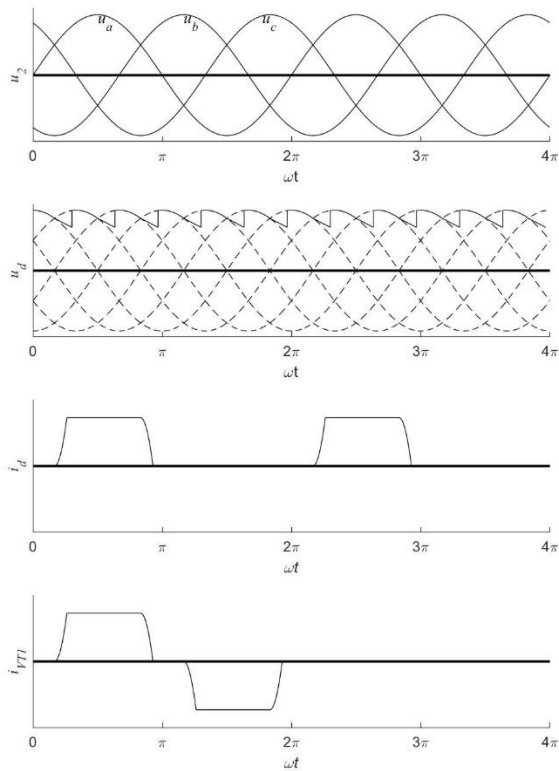
### Answer 3.16

The waveform of  $u_d$ ,  $i_{VD}$ , and  $i_2$ :



A three-phase bridge uncontrolled rectifier circuit is equivalent to A three-phase bridge controlled rectifier circuit with  $\alpha = 0$ .

$$\begin{cases} U_d = 2.34U_2 \cos \alpha - \Delta U_d \\ \Delta U_d = \frac{3X_B I_d}{\pi} \\ I_d = \frac{U_d}{R} \end{cases}$$

Solutions of equations are:

$$\begin{cases} U_d = 486.9V \\ \Delta U_d = 97.38A \end{cases}$$

We can get the relationship that

$$\gamma = 26.93^\circ$$

for the reason that

$$\cos \alpha - \cos(\alpha + \gamma) = \frac{2I_d X_B}{\sqrt{6}U_2}$$

Therefore, the RMS value of the current of diode and the secondary winding of transformer is

$$I_{VD} = \frac{I_d}{3} = \frac{97.38A}{3} = 32.46A$$

$$I_2 = \sqrt{\frac{2}{3}} I_d = \sqrt{\frac{2}{3}} \times 97.38A = 79.5104A$$