

Lecture 8: Solutions for Telegrapher's equations excited by Lumped Source: Green Function

Yan-zhao XIE

Xi'an Jiaotong University

2020.09.24



Recall:

telegrapher's equations

$$\begin{aligned} -\frac{d\tilde{V}(z)}{dz} &= (R' + j\omega L') \tilde{I}(z), \\ -\frac{d\tilde{I}(z)}{dz} &= (G' + j\omega C') \tilde{V}(z). \end{aligned}$$

traveling wave solutions

$$\begin{aligned} \tilde{V}(z) &= V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \\ \tilde{I}(z) &= \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{\gamma z} \end{aligned}$$

reflection coefficient at the load


$$\Gamma_L = \left. \frac{V_0^-}{V_0^+} e^{2\gamma z} \right|_{z=0} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

reflection coefficient along the line

$$\Gamma(z) = \Gamma_L e^{2\gamma z}$$


input impedance
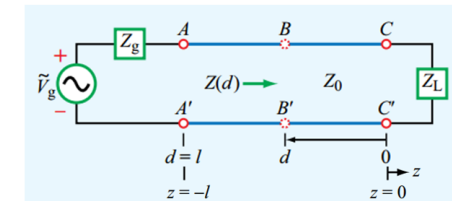
$$Z_{in}(z) = \frac{\tilde{V}(z)}{\tilde{I}(z)} = Z_0 \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$



For a point on the line, one can obtain:
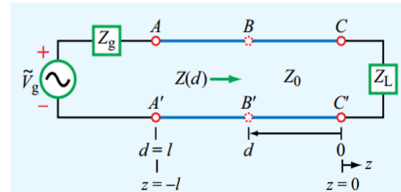
$$\begin{aligned} \tilde{V}(z) &= V_0^+ (e^{-\gamma z} + \Gamma_L e^{\gamma z}) \\ \tilde{I}(z) &= \frac{V_0^+}{Z_0} (e^{-\gamma z} - \Gamma_L e^{\gamma z}) \end{aligned}$$



If we can determine the undetermined constant V_0^+ , then we can evaluate $\tilde{V}(z)$. Knowing boundary conditions, one can specify the exact solutions.

at the source terminal $\tilde{V}(-l) = \tilde{V}_g - Z_g \tilde{I}(-l)$


Substituting the boundary conditions into $\tilde{V}(z)$ and $\tilde{I}(z)$:

$$V_0^+ (e^{\gamma l} + \Gamma_L e^{-\gamma l}) = \tilde{V}_g - Z_g \frac{V_0^+}{Z_0} (e^{\gamma l} - \Gamma_L e^{-\gamma l})$$



One can define the reflection coefficient at the source terminal:
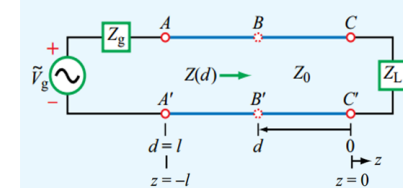
$$\Gamma_g = \frac{Z_g - Z_0}{Z_g + Z_0}$$



$$V_0^+ = \tilde{V}_g \frac{\frac{Z_0}{Z_g + Z_0} e^{-\gamma l}}{1 - \frac{Z_0}{Z_g + Z_0} \Gamma_L e^{-2\gamma l}} = \tilde{V}_g \frac{\frac{1 + \Gamma_g}{2} e^{-\gamma l}}{1 - \Gamma_g \Gamma_L e^{-2\gamma l}}$$


Finally, we can evaluate the exact solutions of $\tilde{V}(z)$ and $\tilde{I}(z)$ while the source is at the terminal of TL:

$$\tilde{V}(z) = \frac{1}{2} \frac{(1 + \Gamma_g) e^{-\gamma l}}{1 - \Gamma_g \Gamma_L e^{-2\gamma l}} (e^{-\gamma z} + \Gamma_L e^{\gamma z}) \tilde{V}_g$$

$$\tilde{I}(z) = \frac{1}{2Z_0} \frac{(1 + \Gamma_g) e^{-\gamma l}}{1 - \Gamma_g \Gamma_L e^{-2\gamma l}} (e^{-\gamma z} - \Gamma_L e^{\gamma z}) \tilde{V}_g$$



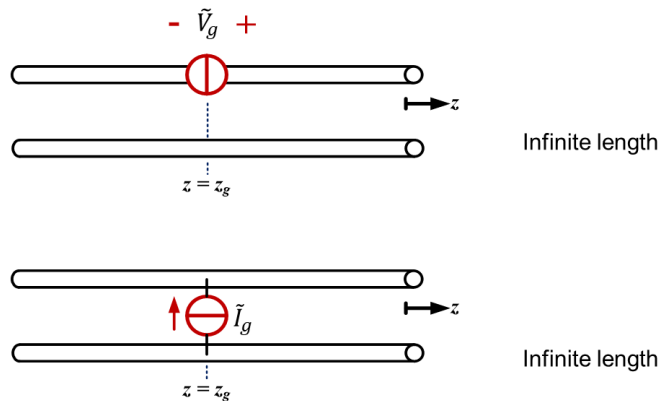
So far, we assume that a lumped source is on a terminal of TL. In fact a lumped source could locate at arbitrary position along TL.



TL excited by a lumped **voltage** source

For $z < z_g$, there is only $V_0^- e^{\gamma z}$, travelling in $-z$ direction.

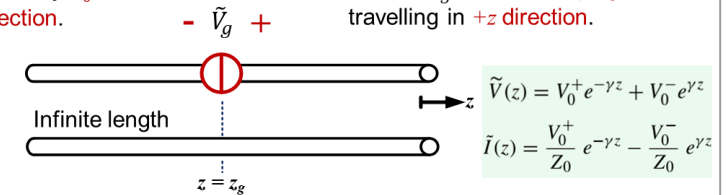For $z > z_g$, there is only $V_0^+ e^{-\gamma z}$, travelling in $+z$ direction.




At $z = z_g$, current is continuous while there is a voltage difference \tilde{V}_g .

$$\begin{aligned} V_0^- e^{\gamma z_g} + \tilde{V}_g &= V_0^+ e^{-\gamma z_g} \\ -\frac{V_0^-}{Z_0} e^{\gamma z_g} &= \frac{V_0^+}{Z_0} e^{-\gamma z_g} \end{aligned} \Rightarrow \begin{aligned} V_0^+ &= \frac{\tilde{V}_g}{2} e^{\gamma z_g} \\ V_0^- &= -\frac{\tilde{V}_g}{2} e^{-\gamma z_g} \end{aligned}$$

$$\text{For } z > z_g, \quad \tilde{V}(z) = \frac{\tilde{V}_g}{2} e^{-\gamma(z-z_g)} \quad \tilde{I}(z) = \frac{\tilde{V}_g}{2Z_0} e^{-\gamma(z-z_g)}$$

$$\text{For } z < z_g, \quad \tilde{V}(z) = -\frac{\tilde{V}_g}{2} e^{\gamma(z-z_g)} \quad \tilde{I}(z) = \frac{\tilde{V}_g}{2Z_0} e^{\gamma(z-z_g)}$$

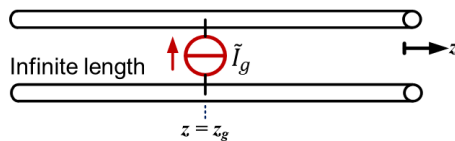TL excited by a lumped **current** source



At $z = z_g$, voltage is continuous while there is a current difference \tilde{I}_g .


Similarly, one can obtain:

$$\text{For } z > z_g, \quad \tilde{V}(z) = \frac{\tilde{I}_g Z_0}{2} e^{-\gamma(z-z_g)} \quad \tilde{I}(z) = \frac{\tilde{I}_g}{2} e^{-\gamma(z-z_g)}$$

$$\text{For } z < z_g, \quad \tilde{V}(z) = \frac{\tilde{I}_g Z_0}{2} e^{\gamma(z-z_g)} \quad \tilde{I}(z) = -\frac{\tilde{I}_g}{2} e^{\gamma(z-z_g)}$$

For $z < z_g$, we rename $\tilde{V}, \tilde{I}, V_0^-$ and V_0^+ as $\tilde{V}_1, \tilde{I}_1, V_1^-$ and V_1^+

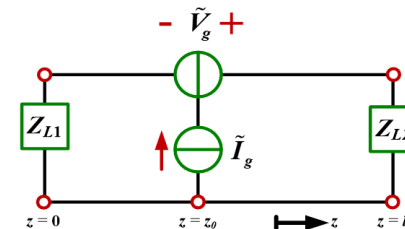For $z > z_g$, we rename $\tilde{V}, \tilde{I}, V_0^-$ and V_0^+ as $\tilde{V}_2, \tilde{I}_2, V_2^-$ and V_2^+



reflection coefficient at two load

$$\Gamma_{L1} = \frac{Z_{L1} - Z_0}{Z_{L1} + Z_0}$$

$$\Gamma_{L2} = \frac{Z_{L2} - Z_0}{Z_{L2} + Z_0}$$

$$\text{Terminal 1: load } Z_{L1} \quad \tilde{V}_1(0) = -\tilde{I}_1(0) \cdot Z_{L1} \Rightarrow V_1^-$$

$$\text{Terminal 2: load } Z_{L2} \quad \tilde{V}_2(l) = \tilde{I}_2(l) \cdot Z_{L2} \Rightarrow V_1^+$$

$$\text{Voltage difference: source } \tilde{V}_g \quad \tilde{V}_1(z_0) + \tilde{V}_g = \tilde{V}_2(z_0) \Rightarrow V_2^-$$

$$\text{Current difference: source } \tilde{I}_g \quad \tilde{I}_1(z_0) + \tilde{I}_g = \tilde{I}_2(z_0) \Rightarrow V_2^+$$

For $z > z_g$,

$$\tilde{V}(z) = \frac{e^{-\gamma z} + \Gamma_{L2} e^{\gamma(z-2l)}}{2(1 - \Gamma_{L1} \Gamma_{L2} e^{-2\gamma l})} [(e^{\gamma z_g} - \Gamma_{L1} e^{-\gamma z_g}) \tilde{V}_g + (e^{\gamma z_g} + \Gamma_{L1} e^{-\gamma z_g}) Z_0 \tilde{I}_g]$$

$$\tilde{I}(z) = \frac{e^{-\gamma z} - \Gamma_{L2} e^{\gamma(z-2l)}}{2Z_0(1 - \Gamma_{L1} \Gamma_{L2} e^{-2\gamma l})} [(e^{\gamma z_g} - \Gamma_{L1} e^{-\gamma z_g}) \tilde{V}_g + (e^{\gamma z_g} + \Gamma_{L1} e^{-\gamma z_g}) Z_0 \tilde{I}_g]$$

For $z < z_g$,

$$\tilde{V}(z) = \frac{e^{\gamma(z-l)} + \Gamma_{L1} e^{-\gamma(z+l)}}{2(1 - \Gamma_{L1} \Gamma_{L2} e^{-2\gamma l})} \left\{ -[e^{\gamma(l-z_g)} - \Gamma_{L2} e^{-\gamma(l-z_g)}] \tilde{V}_g + [e^{\gamma(l-z_g)} + \Gamma_{L2} e^{-\gamma(l-z_g)}] Z_0 \tilde{I}_g \right\}$$

$$\tilde{I}(z) = \frac{e^{\gamma(z-l)} - \Gamma_{L1} e^{-\gamma(z+l)}}{2Z_0(1 - \Gamma_{L1} \Gamma_{L2} e^{-2\gamma l})} \left\{ -[e^{\gamma(l-z_g)} - \Gamma_{L2} e^{-\gamma(l-z_g)}] \tilde{V}_g + [e^{\gamma(l-z_g)} + \Gamma_{L2} e^{-\gamma(l-z_g)}] Z_0 \tilde{I}_g \right\}$$



For $z > z_g$,

$$\tilde{G}_{VV}(z) = \frac{e^{-\gamma z} + \Gamma_{L2} e^{\gamma(z-2l)}}{2(1 - \Gamma_{L1} \Gamma_{L2} e^{-2\gamma l})} (e^{\gamma z_g} - \Gamma_{L1} e^{-\gamma z_g})$$

$$\tilde{G}_{IV}(z) = \frac{e^{-\gamma z} + \Gamma_{L2} e^{\gamma(z-2l)}}{2(1 - \Gamma_{L1} \Gamma_{L2} e^{-2\gamma l})} (e^{\gamma z_g} + \Gamma_{L1} e^{-\gamma z_g}) Z_0$$

$$\tilde{G}_{VI}(z) = \frac{e^{-\gamma z} - \Gamma_{L2} e^{\gamma(z-2l)}}{2Z_0(1 - \Gamma_{L1} \Gamma_{L2} e^{-2\gamma l})} (e^{\gamma z_g} - \Gamma_{L1} e^{-\gamma z_g})$$

$$\tilde{G}_{II}(z) = \frac{e^{-\gamma z} - \Gamma_{L2} e^{\gamma(z-2l)}}{2Z_0(1 - \Gamma_{L1} \Gamma_{L2} e^{-2\gamma l})} (e^{\gamma z_g} + \Gamma_{L1} e^{-\gamma z_g}) Z_0$$

For $z < z_g$,

$$\tilde{G}_{VV}(z) = -\frac{e^{\gamma(z-l)} + \Gamma_{L1} e^{-\gamma(z+l)}}{2(1 - \Gamma_{L1} \Gamma_{L2} e^{-2\gamma l})} [e^{\gamma(l-z_g)} - \Gamma_{L2} e^{-\gamma(l-z_g)}]$$

$$\tilde{G}_{IV}(z) = \frac{e^{\gamma(z-l)} + \Gamma_{L1} e^{-\gamma(z+l)}}{2(1 - \Gamma_{L1} \Gamma_{L2} e^{-2\gamma l})} [e^{\gamma(l-z_g)} + \Gamma_{L2} e^{-\gamma(l-z_g)}] Z_0$$

$$\tilde{G}_{VI}(z) = -\frac{e^{\gamma(z-l)} - \Gamma_{L1} e^{-\gamma(z+l)}}{2Z_0(1 - \Gamma_{L1} \Gamma_{L2} e^{-2\gamma l})} [e^{\gamma(l-z_g)} - \Gamma_{L2} e^{-\gamma(l-z_g)}]$$

$$\tilde{G}_{II}(z) = \frac{e^{\gamma(z-l)} - \Gamma_{L1} e^{-\gamma(z+l)}}{2Z_0(1 - \Gamma_{L1} \Gamma_{L2} e^{-2\gamma l})} [e^{\gamma(l-z_g)} + \Gamma_{L2} e^{-\gamma(l-z_g)}] Z_0$$

$$\tilde{V}(z) = \tilde{G}_{VV}(z) \tilde{V}_g + \tilde{G}_{IV}(z) \tilde{I}_g$$

$$\tilde{I}(z) = \tilde{G}_{VI}(z) \tilde{V}_g + \tilde{G}_{II}(z) \tilde{I}_g$$



Especially, one can obtain the voltage and current at terminals.

For $z = 0$,

$$\tilde{V}(0) = \frac{(1 + \Gamma_{L2}) e^{-\gamma l}}{2(1 - \Gamma_{L1} \Gamma_{L2} e^{-2\gamma l})} [(e^{\gamma z_g} - \Gamma_{L1} e^{-\gamma z_g}) \tilde{V}_g + (e^{\gamma z_g} + \Gamma_{L1} e^{-\gamma z_g}) Z_0 \tilde{I}_g]$$

$$\tilde{I}(0) = \frac{(1 - \Gamma_{L2}) e^{-\gamma l}}{2Z_0(1 - \Gamma_{L1} \Gamma_{L2} e^{-2\gamma l})} [(e^{\gamma z_g} - \Gamma_{L1} e^{-\gamma z_g}) \tilde{V}_g + (e^{\gamma z_g} + \Gamma_{L1} e^{-\gamma z_g}) Z_0 \tilde{I}_g]$$



For $z = l$,

$$\tilde{V}(l) = \frac{(1 + \Gamma_{L1}) e^{-\gamma l}}{2(1 - \Gamma_{L1} \Gamma_{L2} e^{-2\gamma l})} \left\{ -[e^{\gamma(l-z_g)} - \Gamma_{L2} e^{-\gamma(l-z_g)}] \tilde{V}_g + [e^{\gamma(l-z_g)} + \Gamma_{L2} e^{-\gamma(l-z_g)}] Z_0 \tilde{I}_g \right\}$$

$$\tilde{I}(l) = \frac{(1 - \Gamma_{L1}) e^{-\gamma l}}{2Z_0(1 - \Gamma_{L1} \Gamma_{L2} e^{-2\gamma l})} \left\{ -[e^{\gamma(l-z_g)} - \Gamma_{L2} e^{-\gamma(l-z_g)}] \tilde{V}_g + [e^{\gamma(l-z_g)} + \Gamma_{L2} e^{-\gamma(l-z_g)}] Z_0 \tilde{I}_g \right\}$$



Example:

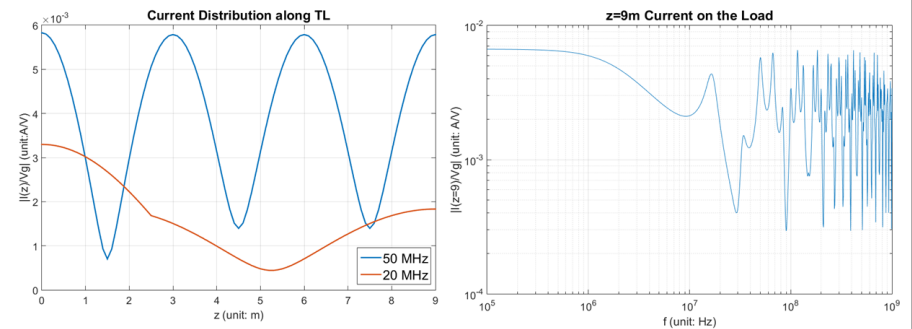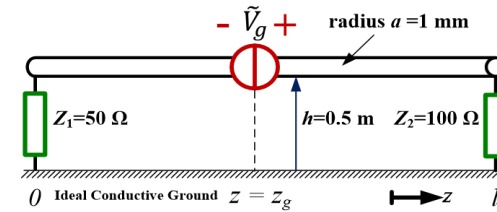

quote

*We make a living by what we get.
We make a life by what we give.*



Thank you again!

