

Lecture 6: Reflection Coefficient


Yan-zhao XIE

Xi'an Jiaotong University

2020.09.22



Recall: General solution

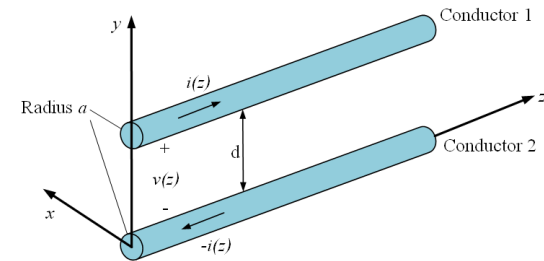

telegrapher's equation

$$\begin{aligned} -\frac{d\tilde{V}(z)}{dz} &= (R' + j\omega L') \tilde{I}(z), \\ -\frac{d\tilde{I}(z)}{dz} &= (G' + j\omega C') \tilde{V}(z). \end{aligned}$$

traveling wave solutions

$$\begin{aligned} \tilde{V}(z) &= V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \\ \tilde{I}(z) &= \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{\gamma z} \end{aligned}$$

propagation constant

$$\gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')} = \sqrt{Z' \cdot Y'}$$




Reflection coefficient

In order to incorporate the **source and load condition** (boundary condition) into the general wave solution, we define a **voltage reflection coefficient $\Gamma(z)$** as the ratio of the reflected and incident voltage waves

$$\Gamma(z) \stackrel{\text{def}}{=} \frac{V_0^- e^{\gamma z}}{V_0^+ e^{-\gamma z}} = \frac{V_0^-}{V_0^+} e^{2\gamma z} \quad \text{How to evaluate } V_0^-/V_0^+ ?$$

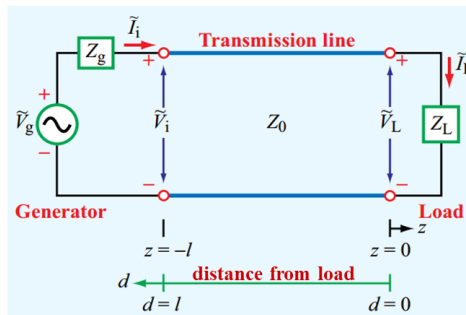One notices the direction of current: $\Gamma(z) = -\frac{I_0^-}{I_0^+} e^{2\gamma z}$



Considering the transmission line in the context of the complete circuit, including:

A generator circuit at its input terminals ($z = -l$)

A l -length TL ($l \leq z \leq 0$)

A load terminated at the output ($z = 0$)




Reflection coefficient

The ratio of the reflected and incident voltage waves is known as the **voltage reflection coefficient $\Gamma(z)$** .

$$\Gamma(z) \stackrel{\text{def}}{=} \frac{V_0^- e^{\gamma z}}{V_0^+ e^{-\gamma z}} = \frac{V_0^-}{V_0^+} e^{2\gamma z} \quad \text{How to evaluate } V_0^-/V_0^+ ?$$

One notices the direction of current:
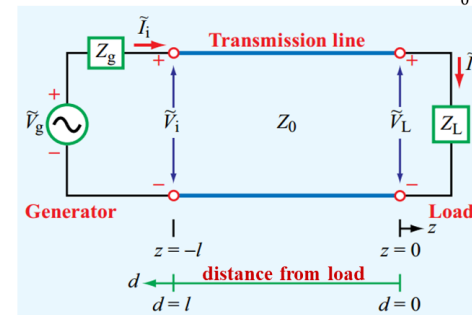
$$\Gamma(z) = -\frac{I_0^-}{I_0^+} e^{2\gamma z}$$




In this case, we define the coordinate:

$$-l \leq z \leq 0$$

generator at the input ($z = -l$);
load at the output ($z = 0$).



Reflection coefficient

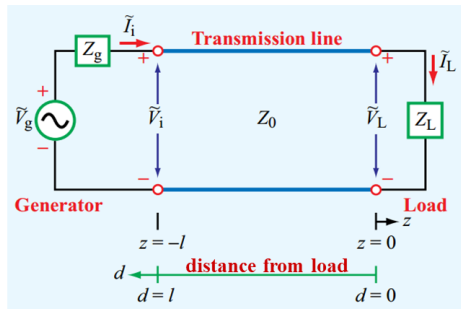

load impedance

$$Z_L = \frac{\tilde{V}(0)}{\tilde{I}(0)} = \frac{V_0^+ + V_0^-}{\frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0}} = \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} Z_0$$



$$\frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Therefore, the reflection coefficient along the line is:

$$\Gamma(z) = \frac{V_0^-}{V_0^+} e^{2\gamma z} = \frac{Z_L - Z_0}{Z_L + Z_0} e^{2\gamma z} = \Gamma_L e^{2\gamma z}$$

Especially, the reflection coefficient at the load :

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$




Γ_L for matched, open, short circuit

Reflection coefficient at the load

$$\Gamma_L \stackrel{\text{def}}{=} \frac{Z_L - Z_0}{Z_L + Z_0}$$

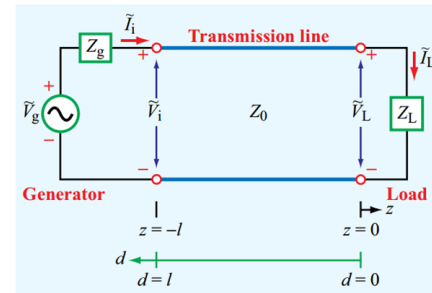A load is said to be **matched** to a transmission line if $Z_L = Z_0$ because there will be no reflection by the load ($\Gamma_L = 0$ and $V_0^- = 0$).



open circuit ($Z_L = \infty$), $\Gamma_L = 1$ and $V_0^- = V_0^+$

short circuit ($Z_L = 0$), $\Gamma_L = -1$ and $V_0^- = -V_0^+$

matched ($Z_L = Z_0$), $\Gamma_L = 0$ and $V_0^- = 0$



Γ_L for various types of load

In general, Z_L is a complex quantity $Z_L = R + jX$, therefore, $\Gamma_L = |\Gamma_L| e^{j\theta_r}$

Load	$ \Gamma $	θ_r
Z_0 $Z_L = (r + jx)Z_0$	$\left[\frac{(r-1)^2 + x^2}{(r+1)^2 + x^2} \right]^{1/2}$	$\tan^{-1} \left(\frac{x}{r-1} \right) - \tan^{-1} \left(\frac{x}{r+1} \right)$
Z_0 Z_0	0 (no reflection)	irrelevant
Z_0 (short)	1	$\pm 180^\circ$ (phase opposition)
Z_0 (open)	1	0 (in-phase)
Z_0 $jX = j\omega L$	1	$\pm 180^\circ - 2 \tan^{-1} x$
Z_0 $jX = \frac{-j}{\omega C}$	1	$\pm 180^\circ + 2 \tan^{-1} x$

$$z_L = Z_L / Z_0 = (R + jX) / Z_0 = r + jx$$

$r = R/Z_0$ and $x = X/Z_0$ are the real and imaginary parts of z_L , respectively.



Thank you!

