

Seminar #2 Report

EE810 Nie Yongxin 2186113564

Topic 1

1. Topic 1

This topic consists of three parts, which are both regarding phase-shifting angle φ . For these three parts, we carried out simulations with Simulink.

2. Simulation Model

In this part, the simulation is regarding series connection of 2 single-phase VSIs with single-phase full bridge inverter, and the simulation is based on the circuit diagram shown below.

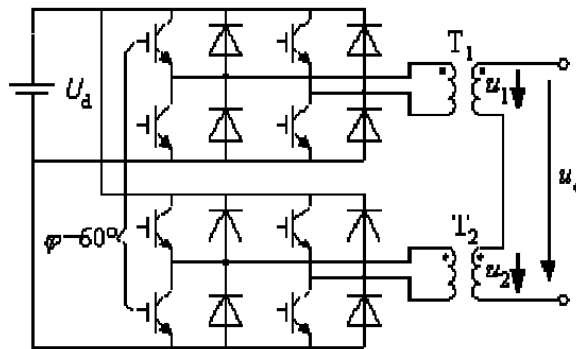


Fig. 1-1 Series connection of 2 single-phase VSIs with single-phase full bridge inverter

We used the model to carry out simulation and then we are required to change the external phase-shifting angle φ between inverters to observe characteristics about the circuit.

2.1 Circuit diagram

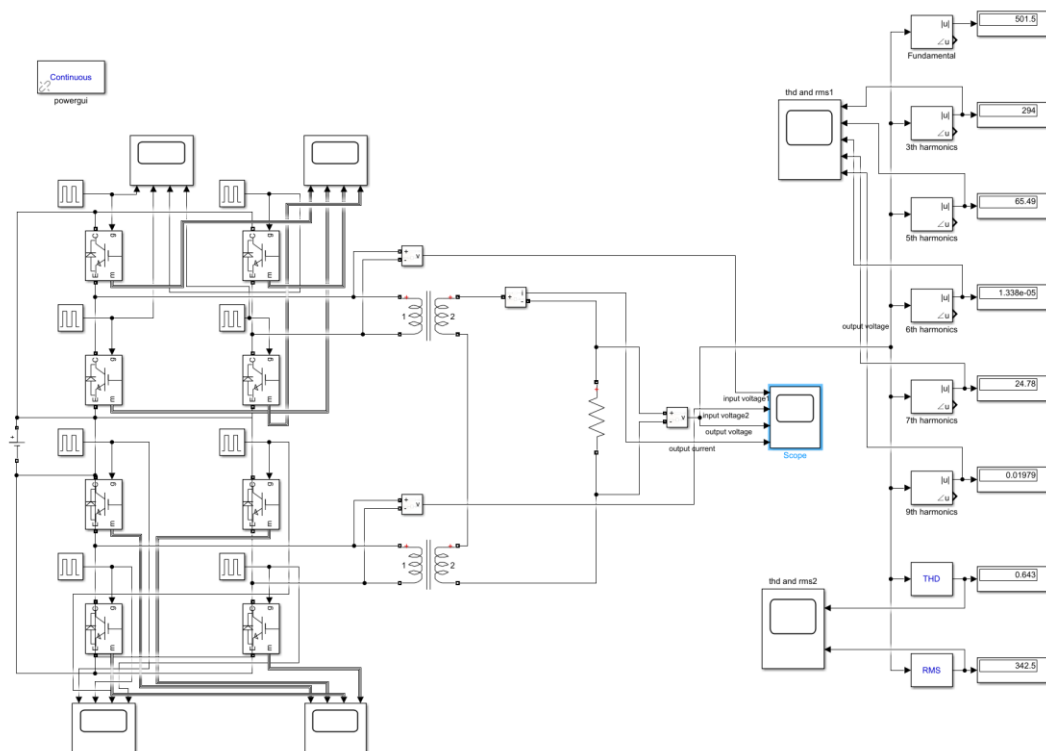


Fig. 1-2 Simulation model

2.2 Task 1

2.2.1 Task requirement

Observe the single inverter's time sequence waveform and input/output voltage relationships.

2.2.2 Time sequence waveform

When we set $\theta = 60^\circ$, for the full-bridge inverter, four IGBTs are conducted by for triggering pulses respectively. The pulse trigger waveforms of V_1 to V_4 are shown below.

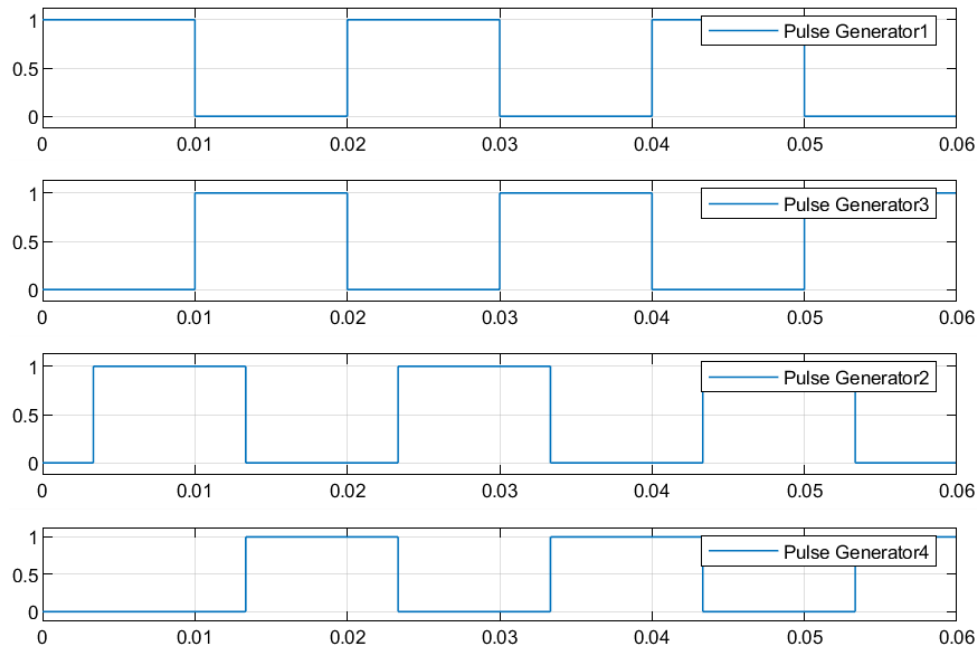


Fig. 1-3 Pulse trigger waveforms of V_1 to V_4

By visual inspection, we can get the four switches are conducted in turn and the sequence is $V_1 \rightarrow V_3 \rightarrow V_2 \rightarrow V_4$. (In the simulation, power diode and IGBT are in the same block, so when either diode or IGBT is conducting, the switch will be at on state.)

2.2.3 Input/output voltage relationship

Firstly, we set $\varphi = 20^\circ$, and the waveforms of input and output are shown in fig. 1-4.

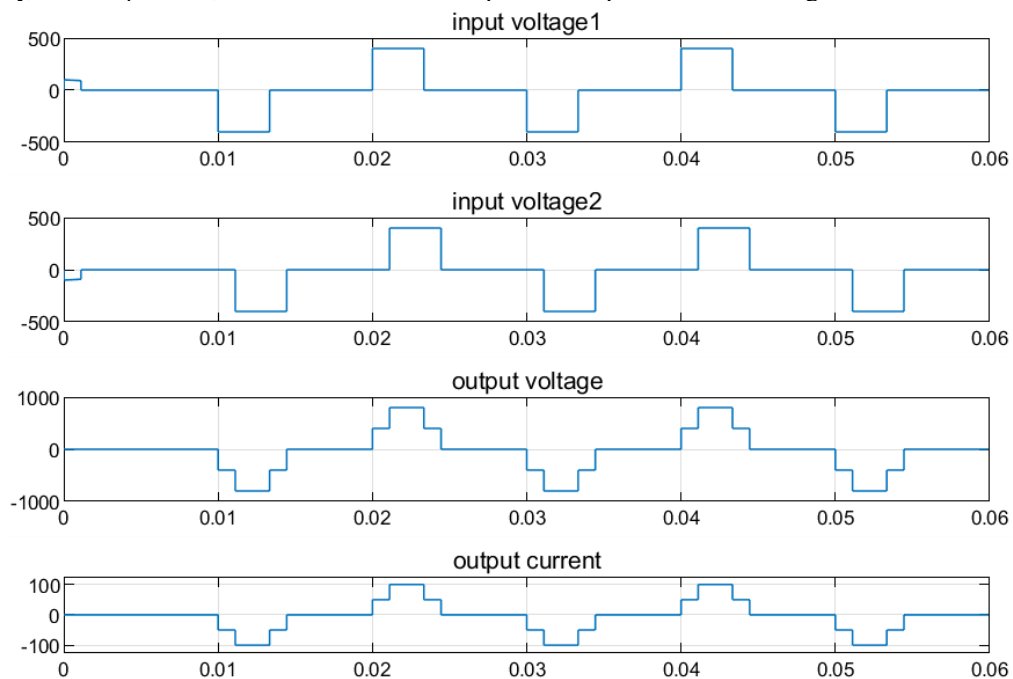


Figure 1-4 input voltage signal and output voltage and current signal

Then, we set $\varphi = 60^\circ$, and the waveforms of input and output are shown in fig. 1-5.

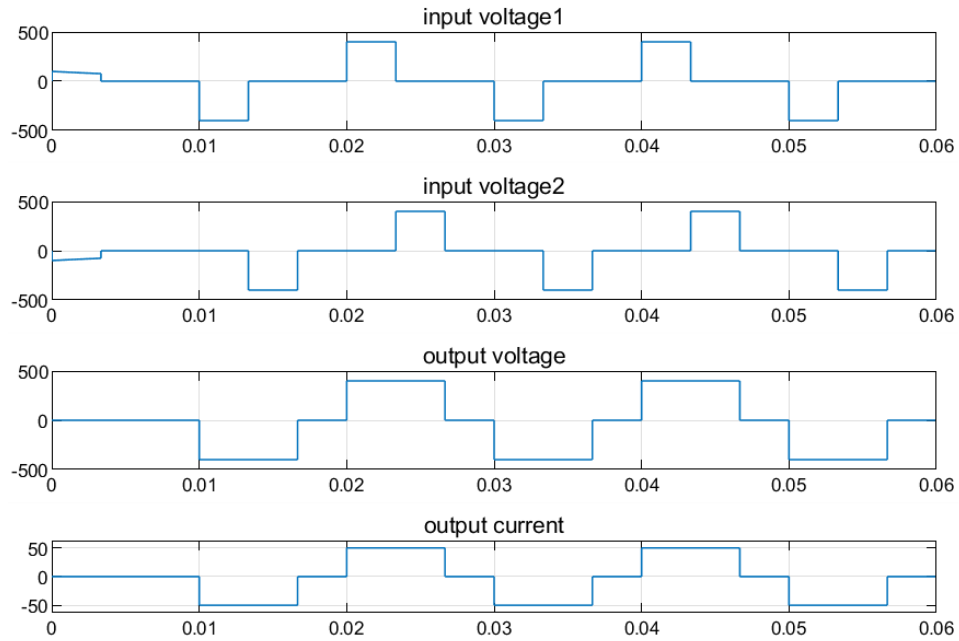


Figure 1-5 input voltage signal and output voltage and current signal

From the figure, we can discover for the 2 single-phase VSIs, the output voltage of inverter equals to the superposition of output voltage of each single-phase VSI.

$$u_o = u_1 + u_2$$

2.3 Task 2

2.3.1 Task requirement

Study the basic operating principle of series connection of multiple single-phase VSIs.

2.3.2 Operating principle

Series connection of multiple single-phase VSIs consists of two single-phase full-bridge inverters and they are connected by transformer T_1 and T_2 . From Task1, we have already known that the output voltage of inverter equals to the superposition of output voltage of each single-phase VSI. Besides, we can change the output waveform by changing the external phase-shifting angle φ .

In figure 1-5 to 1-7, we get the input and output waveform when φ equals to $20^\circ, 60^\circ, 80^\circ$ respectively.

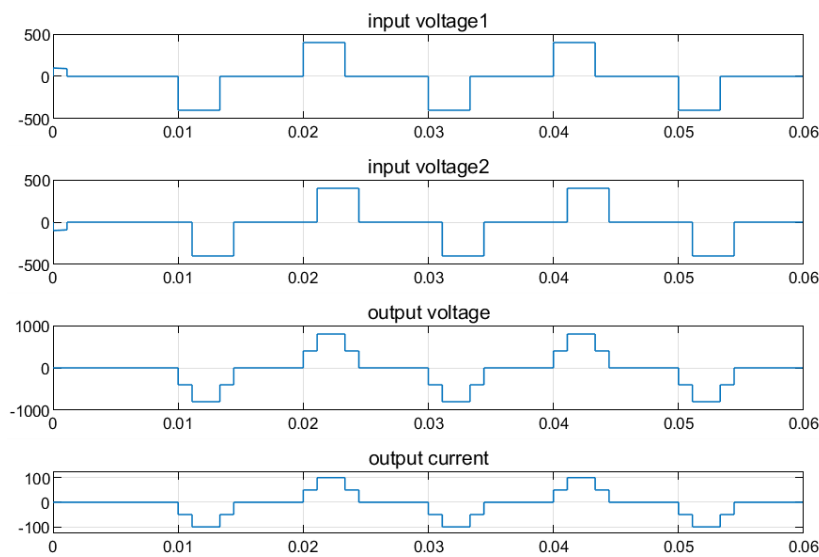


Figure 1-5 input voltage signal and output voltage and current signal $\varphi = 20^\circ$

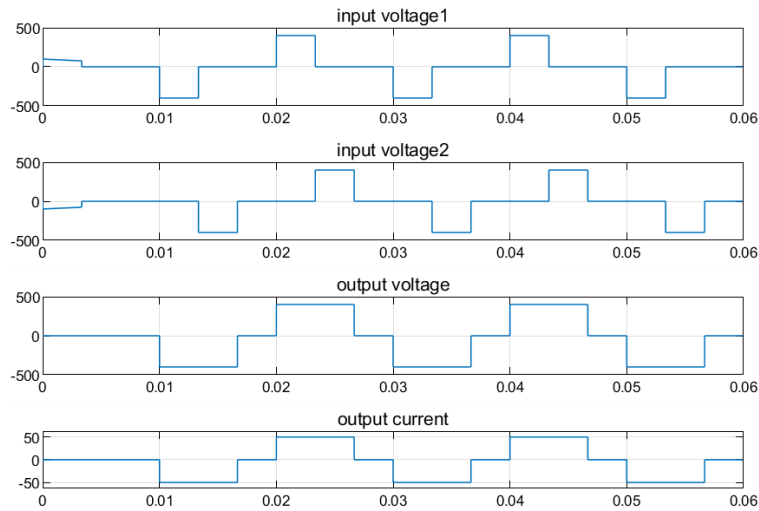


Figure 1-6 input voltage signal and output voltage and current signal $\varphi = 60^\circ$
 In our circuit $\theta = 60^\circ$, so the first critical angle is $120^\circ (180^\circ - 60^\circ = 120^\circ)$. When external phase-shifting angle is within the interval of $0^\circ \sim 120^\circ$, the proportion of zero part in output voltage is decreasing, i.e. the duty cycle is increasing.

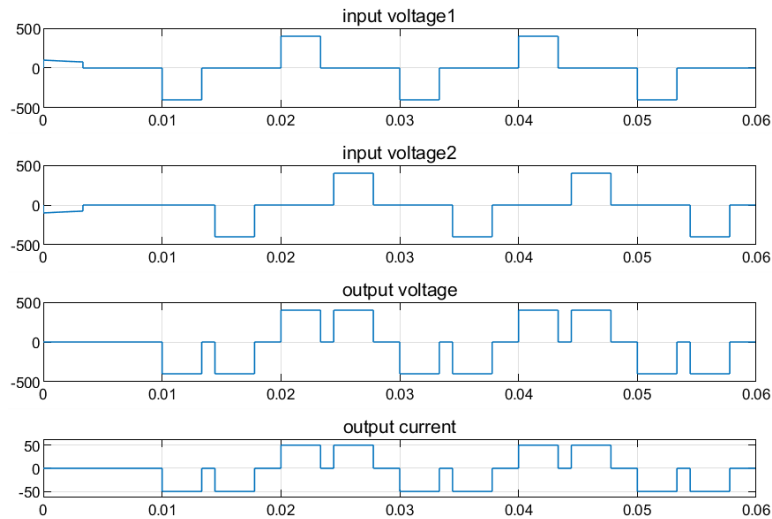


Figure 1-6 input voltage signal and output voltage and current signal $\varphi = 80^\circ$

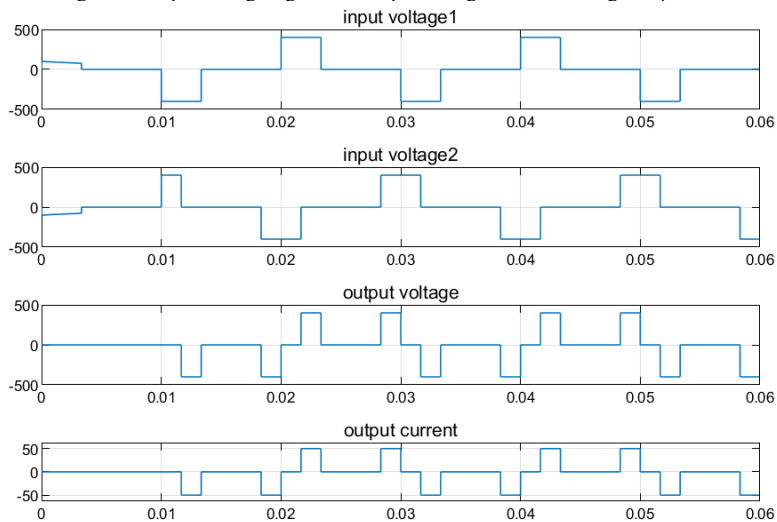


Figure 1-7 input voltage signal and output voltage and current signal $\varphi = 150^\circ$

If $\varphi = 180^\circ$, we can see the output voltage is constant zero.

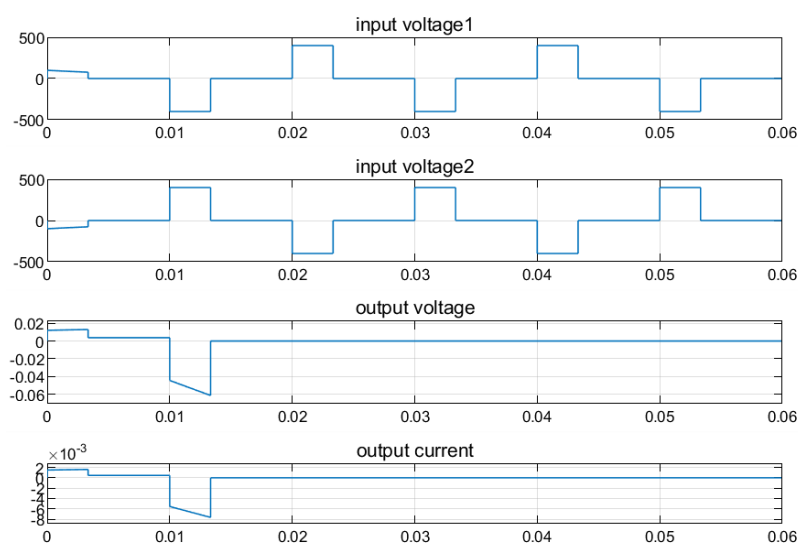


Figure 1-8 input voltage signal and output voltage and current signal $\varphi = 180^\circ$

When external phase-shifting angle is within the interval of $60^\circ \sim 180^\circ$, the proportion of zero part in output voltage is increasing, i.e. the duty cycle is decreasing. In this part, we get the second critical angle $\varphi = 60^\circ$. When $\varphi < 60^\circ$, with φ increases, the shape of output voltage changes little. We can get in Fig. 1-6 to 1-8, 60° is the critical angle of shape change of waveform.

And, during the interval of $180^\circ \sim 360^\circ$, the regularity of output is symmetrical to the interval of $0^\circ \sim 180^\circ$.

Then, we do harmonic analysis. From the one period waveform of u_1 in Fig. 1-7, we can get the Fourier coefficient of u_1 .

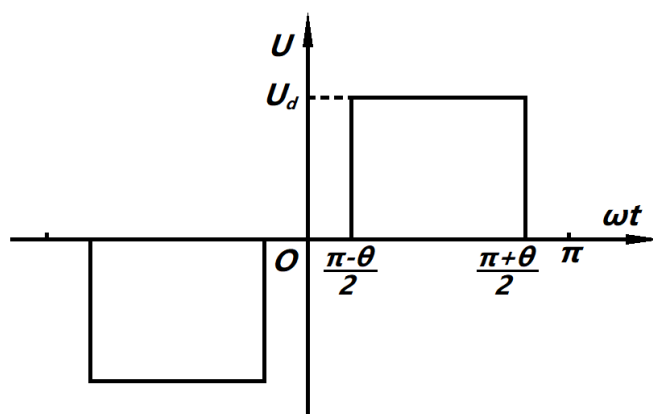


Fig. 1-7 One period of u_1

$$a_n = \frac{2}{\pi} \int_{\frac{\pi-\theta}{2}}^{\frac{\pi+\theta}{2}} U_d \sin nx dx = \frac{4U_d}{n\pi} \sin \frac{n\pi}{2} \sin \frac{n\theta}{2}$$

Therefore, we can get the Fourier series of u_1 and u_2 as below.

$$u_1 = \sum_{n=1}^{\infty} \frac{4U_d}{n\pi} \sin \frac{n\pi}{2} \sin \frac{n\theta}{2} \sin n\omega t$$

$$u_2 = \sum_{n=1}^{\infty} \frac{4U_d}{n\pi} \sin \frac{n\pi}{2} \sin \frac{n\theta}{2} \sin n(\omega t - \varphi)$$

Then, we can get u_o .

$$\begin{aligned} u_o = u_1 + u_2 &= \sum_{n=1}^{\infty} \frac{4U_d}{n\pi} \sin \frac{n\pi}{2} \sin \frac{n\theta}{2} [\sin n\omega t + \sin n(\omega t - \varphi)] \\ &= \sum_{n=1}^{\infty} \frac{8U_d}{n\pi} \sin \frac{n\pi}{2} \sin \frac{n\theta}{2} \cos \frac{n\varphi}{2} \sin \frac{n(2\omega t - \varphi)}{2} \end{aligned}$$

Due to $\sin \frac{n\pi}{2}$, there is no even harmonics in the output.

For instance, we set $\varphi = 60^\circ, \theta = 60^\circ$, and we will get the *Fourier* series of output as below.

$$\begin{aligned} u_1 &= \sum_{n=1}^{\infty} \frac{4U_d}{n\pi} \sin n\omega t \\ u_2 &= \sum_{n=1}^{\infty} \frac{4U_d}{n\pi} \sin n\left(\omega t - \frac{\pi}{3}\right) \quad n = 1, 3, 5, \dots \\ u_o = u_1 + u_2 &= \sum_{n=1}^{\infty} \frac{4U_d}{n\pi} \left[\sin n\omega t + \sin n\left(\omega t - \frac{\pi}{3}\right) \right] \\ &= \frac{4\sqrt{3}U_d}{\pi} \left[\sin\left(\omega t - \frac{\pi}{6}\right) - \frac{1}{5} \sin 5\left(\omega t - \frac{\pi}{6}\right) - \frac{1}{7} \sin 7\left(\omega t - \frac{\pi}{6}\right) + \frac{1}{11} \sin 11\left(\omega t - \frac{\pi}{6}\right) \right. \\ &\quad \left. + \frac{1}{13} \sin 13\left(\omega t - \frac{\pi}{6}\right) - \dots \right] \end{aligned}$$

u_o only has $6k \pm 1^{th} (k = 1, 2, 3, \dots)$ harmonic components while $3k^{th} (k = 1, 2, 3, \dots)$ harmonic components are all counteracted.

As for the third harmonic component of u_1 and u_2 , when we set the external phase-shifting angle $\varphi = 60^\circ$, the phase deviation of third harmonic component is $3 \times 60^\circ = 180^\circ$. Therefore, through the series connection of two transformers, the third harmonic components of u_1 and u_2 are counteracted and u_o doesn't have the third harmonic component. Similarly, $3k^{th} (k = 1, 2, 3, \dots)$ harmonic components are all counteracted.

So, if we combine some output of inverters as definite phase deviation and make some main harmonic components of them counteracted, we can get the waveform which is very close to sine wave.

2.3 Task 3

2.3.1 Task requirement

Plot the curves characterizing the relationships between external phase-shifting angle φ and:

- 1) RMS value of the fundamental component in output voltage;
- 2) output voltage THD;
- 3) 3rd 5th 6th 7th and 9th harmonics components.

By using scripting language which is shown in appendix, we change φ from 0° to 180° and then get the

curves.

2.3.2 Matlab Program

1. 数据获取

```
result = zeros(1,36);
result1 = zeros(1,36);
result2 = zeros(1,36);
result3 = zeros(1,36);
result4 = zeros(1,36);
result5 = zeros(1,36);
result_THD = zeros(1,36);
result_udrms = zeros(1,36);

for i = 1:1:36
    fai = i*10;
    sim('seminar3_1')
    result(i) = simout.Data(length(simout.Data)-1);
    result1(i) = simout1.Data(length(simout1.Data)-1);
    result2(i) = simout2.Data(length(simout2.Data)-1);
    result3(i) = simout3.Data(length(simout3.Data)-1);
    result4(i) = simout4.Data(length(simout4.Data)-1);
    result5(i) = simout5.Data(length(simout5.Data)-1);
    result_THD(i) = simout_THD.Data(length(simout_THD.Data)-1);
    result_udrms(i) = simout_udrms.Data(length(simout_udrms.Data)-1);
end

save DATA1 result result1 result2 result3 result4 result5 result_THD
result_udrms
```

2. 图像绘制主程序

```
clc;
clear;
close all;

load DATA1
angle = 10:10:360;
rms1 = result;
rms3 = result1;
rms5 = result2;
rms6 = result3;
rms7 = result4;
rms9 = result5;
thd = result_THD;
[fitresult, gof] = createFit1(angle, rms1);

[fitresult, gof] = createFit2(angle, thd);
```

```

figure(4)
subplot(2,2,1);
[fitresult, gof] = createFit_rms3(angle, rms3);
subplot(2,2,2);
[fitresult, gof] = createFit_rms5(angle, rms5);
subplot(2,2,3);
[fitresult, gof] = createFit_rms7(angle, rms7);
subplot(2,2,4);
[fitresult, gof] = createFit_rms9(angle, rms9);
h=suptitle({'the relationships between phase-shifting angle';...
    'and 3^{rd} 5^{th} 6^{th} 7^{th} and 9^{th} harmonics
components'});
set(h,'FontName','Times New Roman');

```

```

figure(5)
[fitresult, gof] = createFit8(angle, rms6)

```

2. 图像绘制函数

```

function [fitresult, gof] = createFit1(angle, rms1)
%CREATEFIT(ANGLE,RMS1)
% Create a fit.
%
% Data for 'untitled fit 1' fit:
%     X Input : angle
%     Y Output: rms1
% Output:
%     fitresult : a fit object representing the fit.
%     gof : structure with goodness-of fit info.
%
% 另请参阅 FIT, CFIT, SFIT.

% 由 MATLAB 于 04-Nov-2020 20:25:51 自动生成

%% Fit: 'untitled fit 1'.
[xData, yData] = prepareCurveData( angle, rms1 );

% Set up fittype and options.
ft = fittype( 'smoothingspline' );

% Fit model to data.
[fitresult, gof] = fit( xData, yData, ft );

% Plot fit with data.

```



```

figure( 'Name', 'u1' );
hold on
plot( fitresult, xData, yData );
hold off
axis([0,360,0,inf]);
xlabel('external phase angle - \phi(\circ)')
ylabel('RMS value of the fundamental component in output voltage(V)', 'fontname', 'times new roma')
title({'the relationships between phase-shifting angle';...
      'and RMS value of the fundamental component in output voltage'});
legend('simulink result of RMS value', 'simulink result fit');
set(gca, 'FontName', 'Times New Roman');
set(findobj('Type', 'line'), 'LineWidth', 1.5)
set(gca, 'XTick', 0:30:360);
grid on

```

(the other functions are similar to this function, they are all using the curve fit tool toolbox in MATLAB, so they are not posted here.)

3. Parameter Setup

Table 1 Distributed parameters

| | |
|-------------------------------|-----------------------------------|
| Inverter type | Single-phase full-bridge inverter |
| Internal phase-shifting angle | $\theta=60^\circ$ |
| V_{DC} | 400V |
| R_{load} | 8Ω |

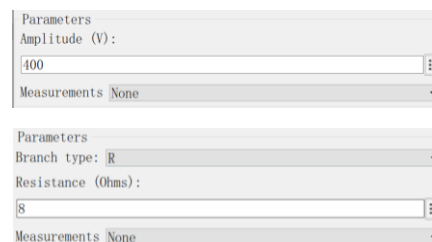


Figure 1-5 parameter setup

From the figure, we can discover for the 2 single-phase VSIs, the output voltage of inverter equals to the superposition of output voltage of each single-phase VSI.

$$u_o = u_1 + u_2$$

4. Analysis of the Results

2.3.2 Relationship between fundamental component and φ

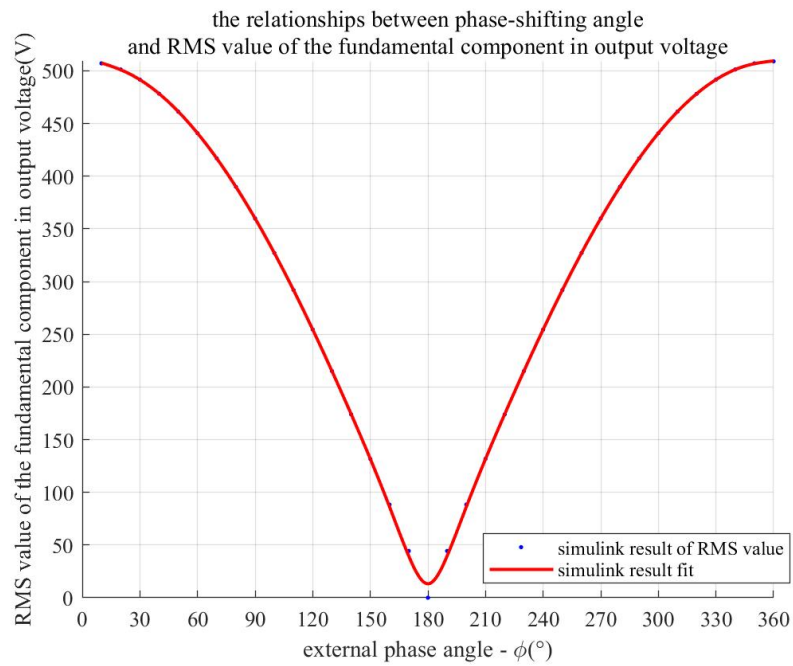


Fig. 1-15 The curve of relationship between fundamental component and φ

The RMS value of fundamental component in output voltage decreases with the increase of φ .

Through Fourier analysis, we can get the RMS of fundamental component in the formula as below:

We can see U_1 is in direct proportion to $\cos \varphi/2$. From the function monotonicity, we can easily get U_1 decreases while φ is increasing.

2.3.3 Relationship between THD and φ

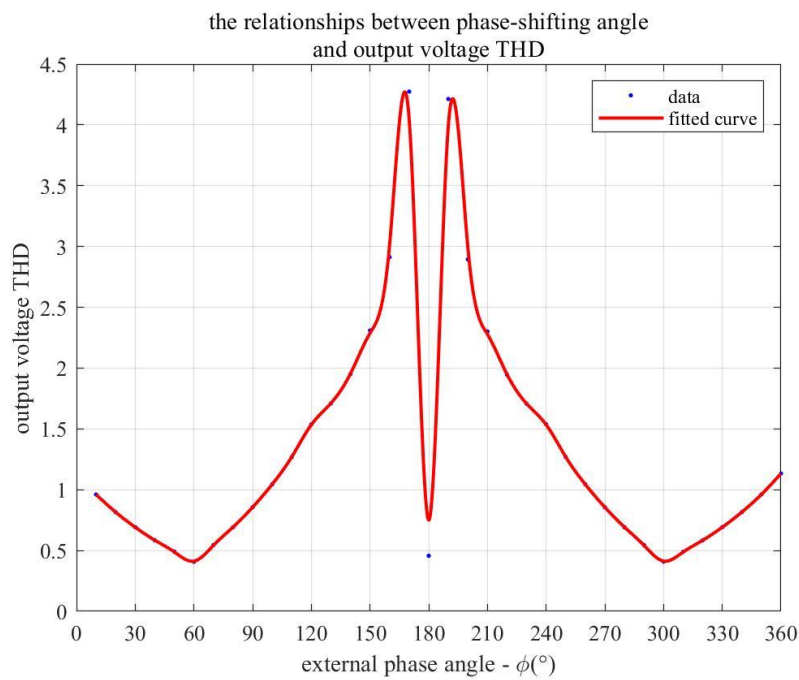


Fig. 1-16 The curve of relationship between THD and φ

The curve decreases during the interval from 0° to 60° and increase rapidly beyond 60° . The reason is that beyond 60° , there is shape change in voltage waveform. Besides, when φ equals to 180° , the output

is constant zero, so THD is non-existent. In the simulation curve, we can see THD is about 0.5 when φ equals to 180° .

And when $\varphi=60^\circ$, the curve gets its minimum value. From Fig. 1-18, 3rd harmonic is the main part in harmonics. At 60° , there is no 3rd harmonic while fundamental component is still very large. Therefore, the THD will get its minimum value.

2.3.4 Relationship between 3rd 5th 6th 7th and 9th harmonics components and φ

In the former discussion, we have known there is no even harmonic in the output. Therefore, we shouldn't have got 6th harmonic component in the simulation. The figure below is the relationship between 6th harmonic component and φ .

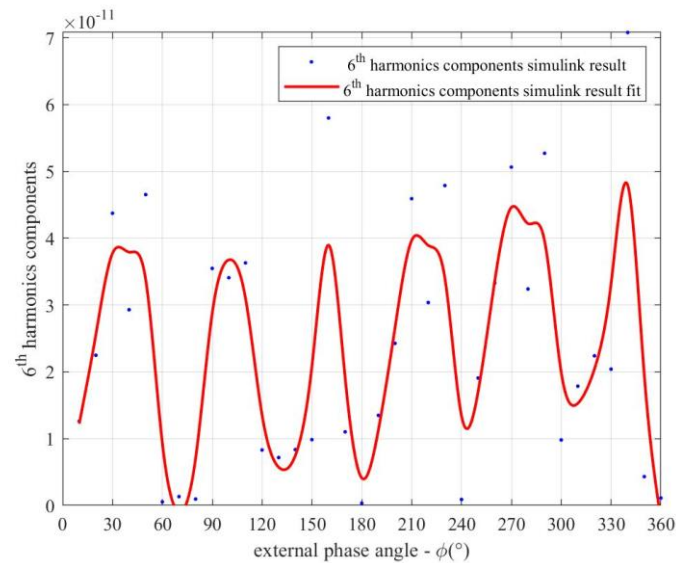


Fig. 1-17 The curve of relationship between 6th harmonic component and φ

In the simulation result, we can see the 6th is nearly zero. However, due to the algorithm of Simulink, there is small fluctuation in the figure.

We also get the curve of relationship between 3rd, 5th, 7th and 9th harmonic component and φ .

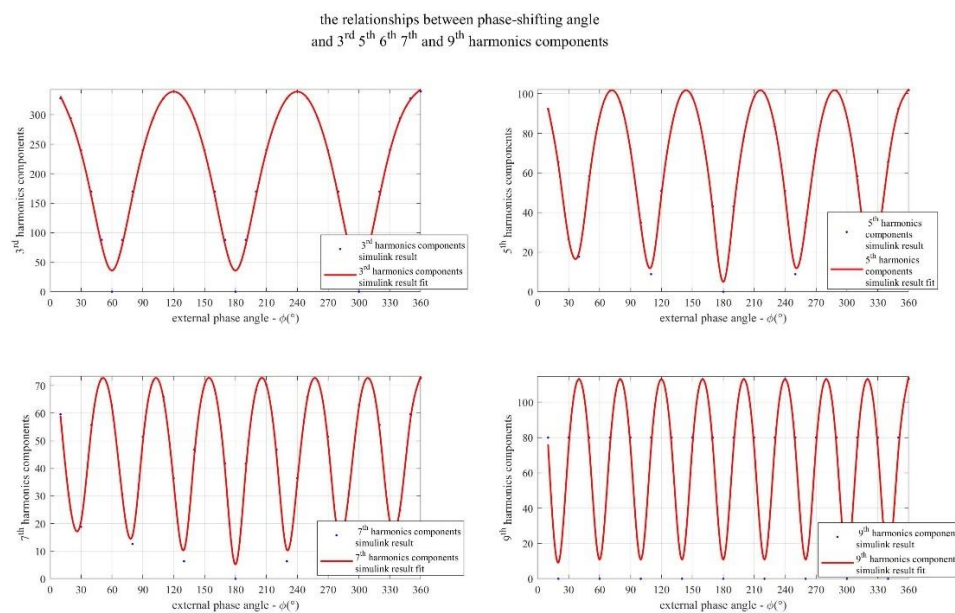


Fig. 1-18 Relationship between 3rd, 5th, 7th and 9th harmonic component and φ

By Fourier analyzation, we can get the peak value of harmonics as below.

$$|U_{nm}| = \frac{8U_d}{n\pi} \left| \sin \frac{n\pi}{2} \sin \frac{n\theta}{2} \cos \frac{n\varphi}{2} \right|$$

We can see the simulation result is the same as theoretical analyzation.

Topic 2

1. Topic 2

In this topic, the simulation is regarding three-phase bridge inverters and the simulation model is shown below.

2. Simulation Model

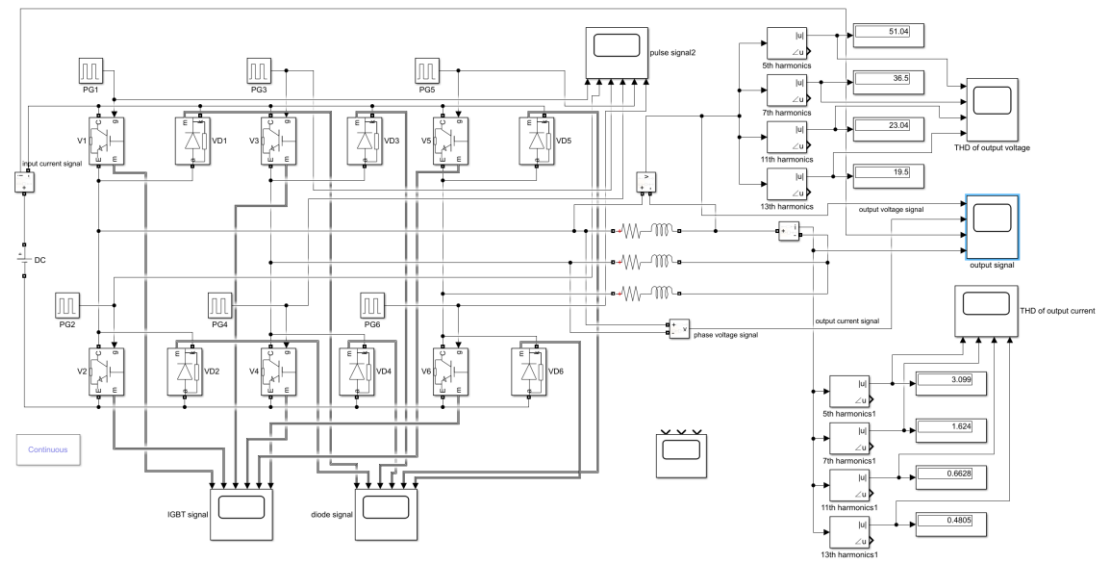


Figure 2-1 Simulation model

3. Parameter Setup

Table 2 Distributed parameters

| Inverter type | Three-phase bridge inverter |
|---------------|-----------------------------|
| f | 50Hz |
| V_{DC} | 200V |
| R_{load} | 5 Ω |
| L | 10mH |

Resistance (Ohms):

5

Inductance (H):

0.01

Parameters

Amplitude (V):

400

Figure 2-7 Parameter setup

| Parameters | |
|----------------------------|---------------------|
| Pulse type: | Time based |
| Time (t): | Use simulation time |
| Amplitude: | 1 |
| Period (secs): | 0.02 |
| Pulse Width (% of period): | 50 |
| Phase delay (secs): | $0.02 * (1/3)$ |

Figure 2-8 Parameter setup

4. Simulation Result

2.2.1 Topic requirement

For three-phase bridge inverter, analyze the voltage across power switch and the current flowing through it. And calculate the 5th 7th 11th and 13th harmonics components in output voltage and output current. Then compare with simulation results.

2.2.2 The output voltage and current

We do the simulation and get the waveform of voltage. Firstly, the waveforms of pulse signal are shown as below.

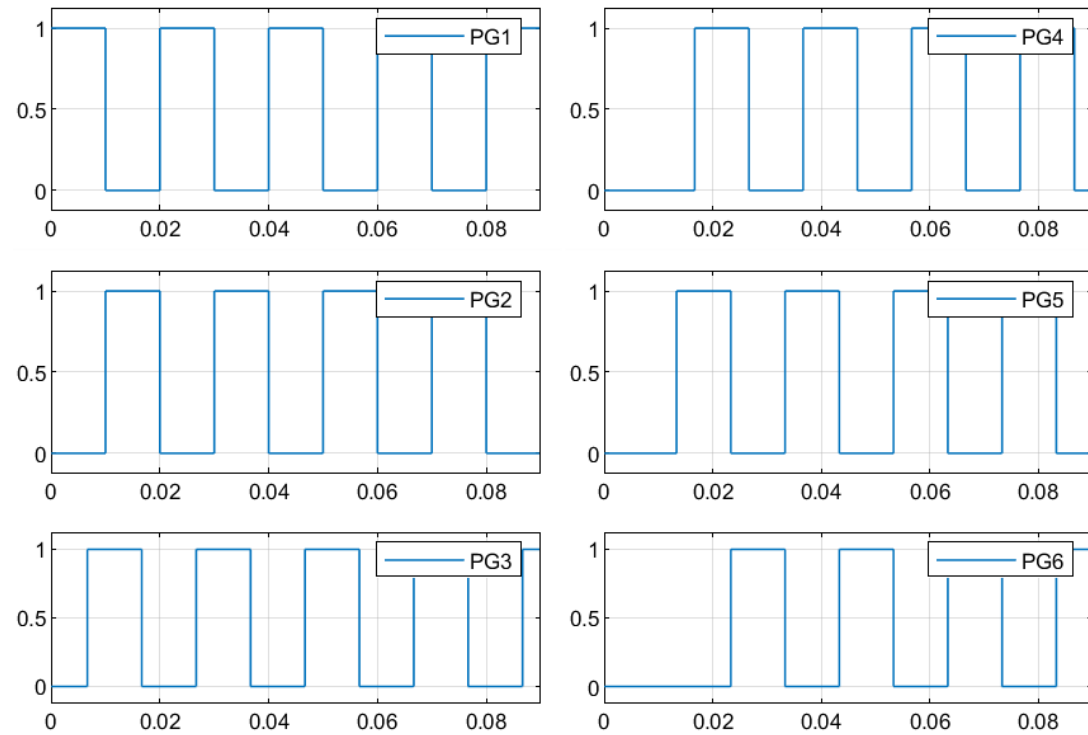


Fig. 2-2 The waveforms of $U_{UN'}$, $U_{VN'}$ and $U_{WN'}$

Secondly, we get Waveform of u_d , u_{uv} , i_d and i_u

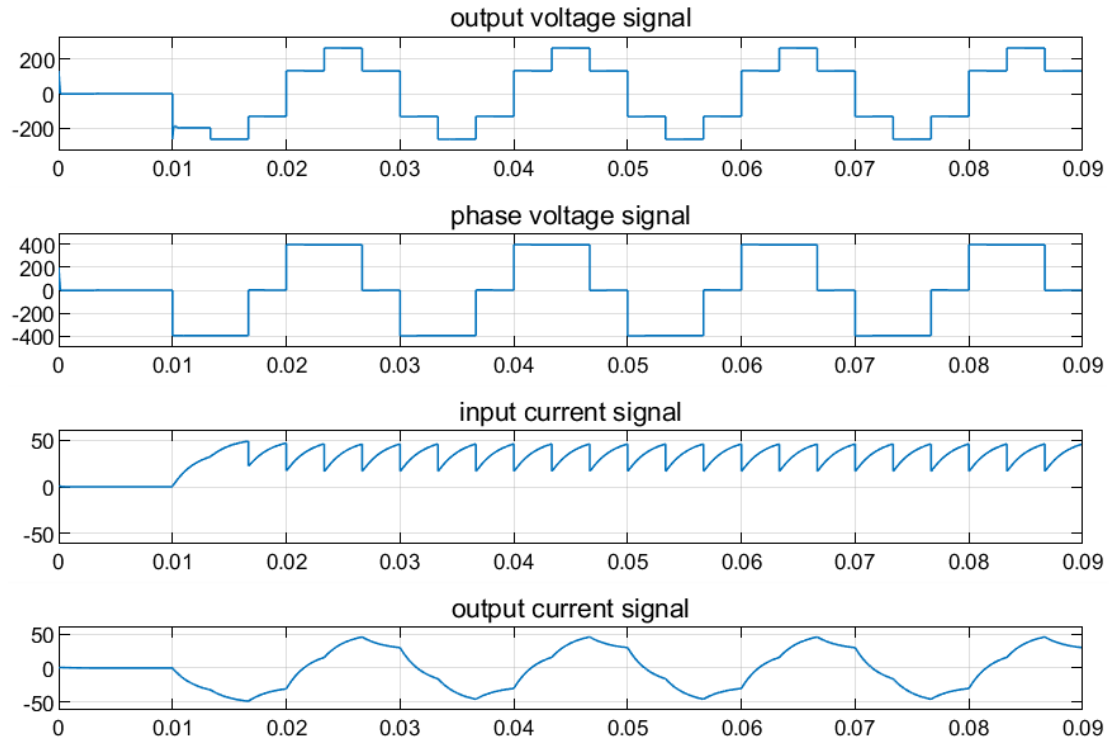


Fig. 2-4 Waveform of u_d , u_{uv} , i_d and i_u

2.2.3 The voltage and current about power switch

These 6 IGBTs are triggered following the order from 1 to 6. The delay of each IGBT is 60° . Each group of IGBTs can be divided into 3 groups (VT1 and VT4, VT3 and VT6, VT5 and VT2). There is only one IGBT of each group conducted at the same time, which means at every moment there will be 3 IGBTs conducted.

Owing to the inductance load, a small part of time of current through each bridge arm is opposite current. And during this small part of time, IGBT is not conducted, in that the free-wheeling diode is conducting current. When the current is positive, IGBT will be conducted. From the figure, we can see there is only one IGBT in this group of bridge arm is conducted during half period.

And the waveform of voltage and current about six bridge arms are shown as below.

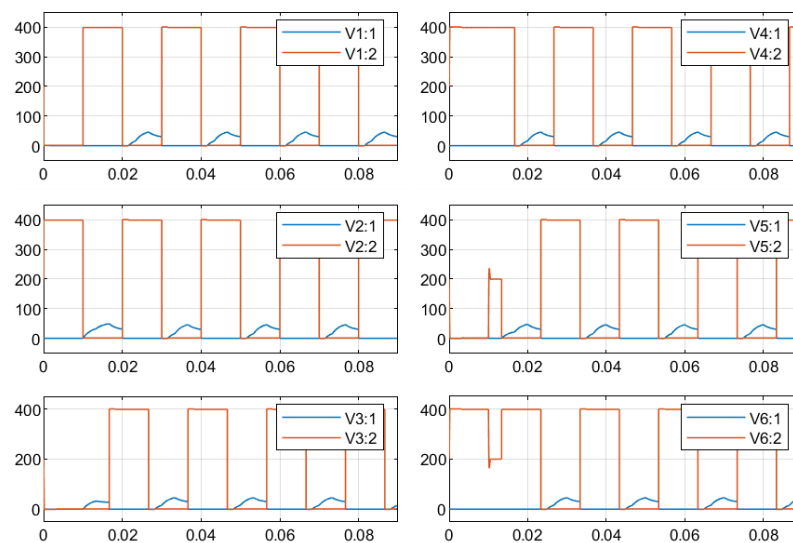


Fig. 2-6 The waveform of voltage and current about 6 IGBTs

5. Analysis of the Results

To avoid the unstable state of the beginning period, we use the scope to observe the harmonics component to make sure that the measurement of harmonics component has reached the stable state.

The waveforms of the output voltage and output current harmonics are shown below.

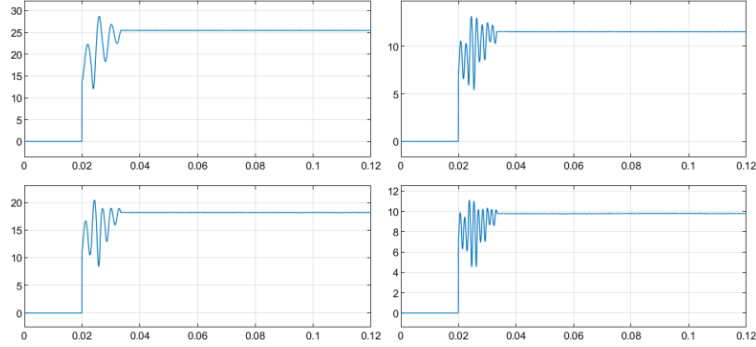


Figure 2-8 the waveform of output voltage harmonics component

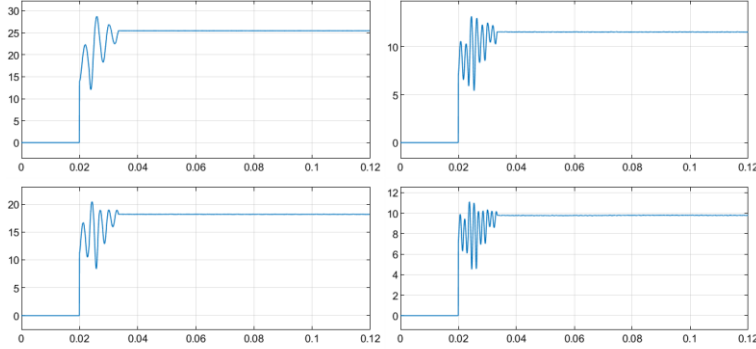


Figure 2-8 the waveform of output current harmonics component

Decompose the output phase voltage u_{UN} to Fourier series:

$$\begin{aligned} u_{UN} &= \frac{2U_d}{\pi} \left[\sin\omega t + \frac{1}{5}\sin 5\omega t + \frac{1}{7}\sin 7\omega t + \frac{1}{11}\sin 11\omega t + \frac{1}{13}\sin 13\omega t - \dots \right] \\ &= \frac{2U_d}{\pi} \left[\sin\omega t + \sum_n \frac{1}{n} \sin n\omega t \right] \\ &\quad (n = 6k \pm 1) \end{aligned}$$

RMS value:

$$U_{UN} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} u_{UN}^2 d\omega t} = 0.471U_d = 0.471 \times 200 = 94.2V$$

From our simulation, we get $U_{UN} = 92.18V$

The fundamental wave of output voltage

$$U_{UN1m} = \frac{2U_d}{\pi} = 127.32395V$$

The simulation value is 127.3240V, and the percentage deviation is nearly 0.

The amplitude value of 5th, 7th, 11th and 13th harmonic components are shown as below.

$$U_{UN5m} = \frac{2U_d}{5\pi} = 25.4648V$$

$$U_{UN7m} = \frac{2U_d}{7\pi} = 18.1891V$$

$$U_{UN11m} = \frac{2U_d}{11\pi} = 11.5749V$$

$$U_{UN13m} = \frac{2U_d}{13\pi} = 9.7942V$$

Table 2 Comparison of simulation value and theoretical value of harmonic components

| Harmonic number | Simulation value | Theoretical value | Percentage deviation |
|-----------------|------------------|-------------------|----------------------|
| 5 | 25.45 | 25.46 | 0.03% |
| 7 | 18.17 | 18.19 | 0.11% |
| 11 | 11.55 | 11.57 | 0.17% |
| 13 | 9.77 | 9.794 | 0.25% |

Then we calculate HRV_n and compare the simulation value and theoretical value.

Table 3 Comparison of simulation value and theoretical value of HRV_n

| Harmonic number | Simulation value | Theoretical value |
|-----------------|------------------|-------------------|
| 5 | 19.91% | 20.00% |
| 7 | 14.32% | 14.29% |
| 11 | 9.06% | 9.09% |
| 13 | 7.69% | 7.69% |

Concluding from the table, there is no obvious difference between simulation value and theoretical value.

2.4 Calculation of harmonic components in output current

Decompose the output phase current I_{UN} to Fourier series and do the calculation.

$$I_{UN1m} = \frac{U_{UN1m}}{\sqrt{R^2 + (\omega_1 L)^2}} = 21.5619A$$

$$I_{UN5m} = \frac{U_{UN5m}}{\sqrt{R^2 + (\omega_5 L)^2}} = 1.5448A$$

$$I_{UN7m} = \frac{U_{UN7m}}{\sqrt{R^2 + (\omega_7 L)^2}} = 0.8065A$$

$$I_{UN11m} = \frac{U_{UN11m}}{\sqrt{R^2 + (\omega_{11} L)^2}} = 0.3315A$$

$$I_{UN13m} = \frac{U_{UN13m}}{\sqrt{R^2 + (\omega_{13} L)^2}} = 0.2380A$$

Table 4 Comparison of simulation value and theoretical value of harmonic components

| Harmonic number | Simulation value | Theoretical value | Percentage deviation |
|-----------------|------------------|-------------------|----------------------|
| 1 | 23.14 | 21.5619 | 7.31% |
| 5 | 1.675 | 1.5448 | 8.42% |
| 7 | 0.9195 | 0.9065 | 1.43% |
| 11 | 0.4028 | 0.3915 | 2.89% |
| 13 | 0.1955 | 0.1980 | 1.26% |

And we calculate HRI_n and compare the simulation value and theoretical value.

$$HRI_n = \frac{1}{n} \sqrt{\frac{R^2 + (\omega_1 L)^2}{R^2 + (\omega_n L)^2}} \times 100\%$$

Table 5 Comparison of simulation value and theoretical value of HRI_n

| Harmonic number | Simulation value | Theoretical value |
|-----------------|------------------|-------------------|
| 5 | 11.23% | 11.26% |
| 7 | 6.22% | 6.20% |
| 11 | 2.66% | 2.65% |
| 13 | 1.93% | 1.92% |

There is no obvious difference between simulation value and theoretical value.