

Lecture 10: Solutions for Telegrapher's equations excited by Lumped Source : Chain Parameter Matrix

Yan-zhao XIE


Xi'an Jiaotong University

2020.09.29




System response

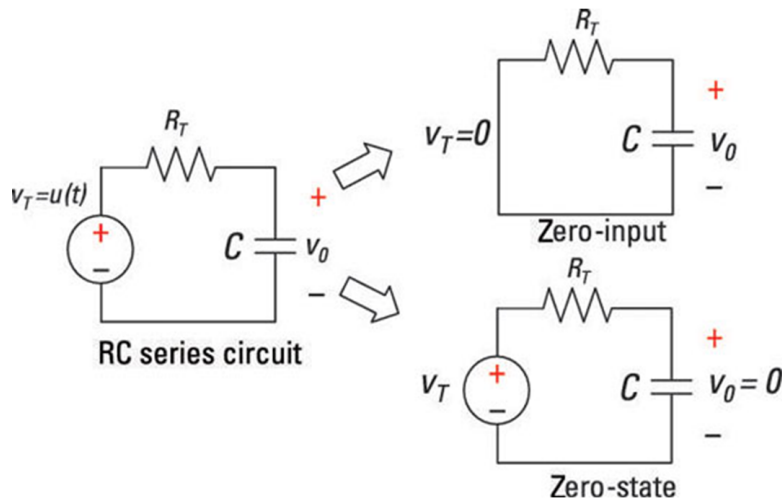- Natural + Forced
- Transient + Steady-state
- Zero-input + Zero-state



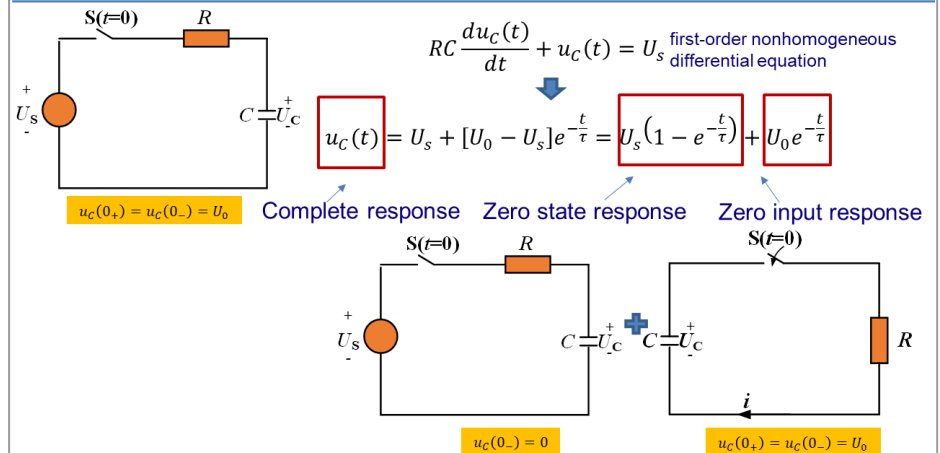Recall: Response of first-order differential circuit



The zero state response (ZSR) is the behavior or response of a circuit with initial state of zero.

The zero input response (ZIR) is the behavior or response of a circuit without external excitation source (forcing source).




<https://www.dummies.com/education/science/science-electronics/find-the-zero-input-and-zero-state-responses-of-a-series-rc-circuit/>



Two-port representation of TL

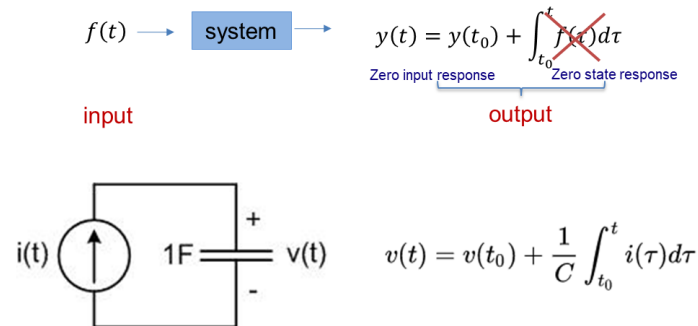
Similarly, when a function is put into a **linear time-invariant (LTI)** system, an output can be characterized by a **superposition or sum** of the **zero input response** and the **zero state response**.



Two-port representation of TL


The independent variable is time t for a **linear time-invariant (LTI)** system whereas the independent variable now is the line axis variable z .

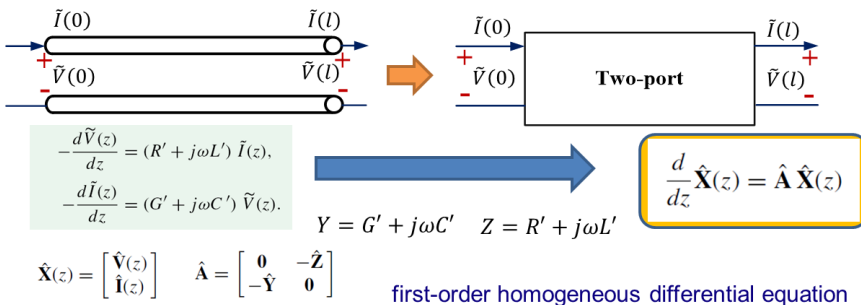Since we are generally not interested in the line voltages and currents at points along the line other than at the **terminations**, we can regard the line as a two-port circuit.



Two-port representation of TL

Zero input response

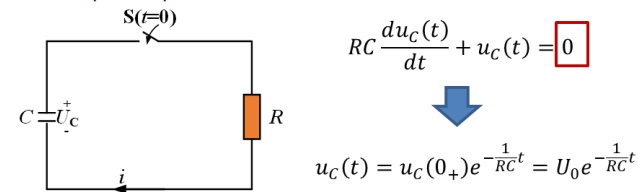

The compact matrix form of the Telegrapher's equations are identical in form to the state-variable equations that describe some linear systems but the independent variable is the line axis variable z instead of time t .

The compact matrix form of the Telegrapher's equations is:

$$\frac{d}{dz} \hat{\mathbf{X}}(z) = \hat{\mathbf{A}} \hat{\mathbf{X}}(z)$$

where $\hat{\mathbf{X}}(z) = \begin{bmatrix} \tilde{V}(z) \\ \tilde{I}(z) \end{bmatrix}$ and $\hat{\mathbf{A}} = \begin{bmatrix} 0 & -\hat{\mathbf{Z}} \\ -\hat{\mathbf{Y}} & 0 \end{bmatrix}$. The parameters $\hat{\mathbf{Y}} = G' + j\omega C'$ and $\hat{\mathbf{Z}} = R' + j\omega L'$ are the admittance and impedance matrices, respectively.

The solution is:

$$\begin{bmatrix} \tilde{V}(l) \\ \tilde{I}(l) \end{bmatrix} = \begin{bmatrix} \tilde{\Phi}_{11}(l) & \tilde{\Phi}_{12}(l) \\ \tilde{\Phi}_{21}(l) & \tilde{\Phi}_{22}(l) \end{bmatrix} \begin{bmatrix} \tilde{V}(0) \\ \tilde{I}(0) \end{bmatrix}$$

The matrix $\tilde{\Phi}(l)$ is the Chain-parameter matrix.



Chain-parameter matrix

To obtain chain-parameter matrix, calculating the general solution at $z=0$ and $z=l$.

$$\begin{aligned} \tilde{V}(z) &= V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \\ \tilde{I}(z) &= \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{\gamma z} \end{aligned} \Rightarrow \begin{aligned} \begin{bmatrix} \tilde{V}(0) \\ \tilde{I}(0) \end{bmatrix} &= \begin{bmatrix} 1 & 1 \\ 1/Z_0 & -1/Z_0 \end{bmatrix} \begin{bmatrix} V_0^+ \\ V_0^- \end{bmatrix} \\ \begin{bmatrix} \tilde{V}(l) \\ \tilde{I}(l) \end{bmatrix} &= \begin{bmatrix} e^{-\gamma l} & e^{\gamma l} \\ e^{-\gamma l}/Z_0 & -e^{\gamma l}/Z_0 \end{bmatrix} \begin{bmatrix} V_0^+ \\ V_0^- \end{bmatrix} \end{aligned} \quad (a) \quad (b)$$

Substituting (a) into (b):

$$\begin{aligned} \begin{bmatrix} \tilde{V}(l) \\ \tilde{I}(l) \end{bmatrix} &= \begin{bmatrix} e^{-\gamma l} & e^{\gamma l} \\ e^{-\gamma l}/Z_0 & -e^{\gamma l}/Z_0 \end{bmatrix} \frac{1}{2} \begin{bmatrix} 1 & Z_0 \\ 1 & -Z_0 \end{bmatrix} \begin{bmatrix} \tilde{V}(0) \\ \tilde{I}(0) \end{bmatrix} \\ &= \begin{bmatrix} \frac{e^{\gamma l} + e^{-\gamma l}}{2} & -Z_0 \frac{e^{\gamma l} - e^{-\gamma l}}{2} \\ -\frac{1}{Z_0} \frac{e^{\gamma l} - e^{-\gamma l}}{2} & \frac{e^{\gamma l} + e^{-\gamma l}}{2} \end{bmatrix} \begin{bmatrix} \tilde{V}(0) \\ \tilde{I}(0) \end{bmatrix} \end{aligned}$$



The Chain-parameter is

$$\begin{aligned} \tilde{\Phi}_{11}(l) &= \frac{e^{\gamma l} + e^{-\gamma l}}{2} = \cosh \gamma l & \tilde{\Phi}_{12}(l) &= -Z_0 \frac{e^{\gamma l} - e^{-\gamma l}}{2} = -jZ_0 \sinh \gamma l \\ \tilde{\Phi}_{21}(l) &= -\frac{1}{Z_0} \frac{e^{\gamma l} - e^{-\gamma l}}{2} = -j \frac{\sinh \gamma l}{Z_0} & \tilde{\Phi}_{22}(l) &= \frac{e^{\gamma l} + e^{-\gamma l}}{2} = \cosh \gamma l \end{aligned}$$

It can also be deduced that: $\tilde{\Phi}(l)\tilde{\Phi}^{-1}(l) = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} = \tilde{\Phi}(l)\tilde{\Phi}(-l)$

$$\tilde{\Phi}^{-1}(l) = \tilde{\Phi}(-l) \Rightarrow \tilde{\Phi}^{-1}(l) = \tilde{\Phi}(-l) = \begin{bmatrix} \tilde{\Phi}_{11}(l) & -\tilde{\Phi}_{12}(l) \\ -\tilde{\Phi}_{21}(l) & \tilde{\Phi}_{22}(l) \end{bmatrix}$$


We can get the inverse relationship:

$$\begin{bmatrix} \tilde{V}(0) \\ \tilde{I}(0) \end{bmatrix} = \tilde{\Phi}(-l) \begin{bmatrix} \tilde{V}(l) \\ \tilde{I}(l) \end{bmatrix}$$

It is a simple reversal of the line axis scale (replacing z with $-z$) similar to the reversal in time for the state-transition matrix of lumped systems.



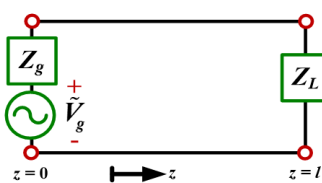The chain parameters only relate the voltage and current **at one end of the line** to the voltage and current **at the other end of the line**. They do not explicitly determine those voltages and currents until we incorporate the terminals conditions.



boundary conditions:

$$\tilde{V}(0) = \tilde{V}_g - Z_g \tilde{I}(0) \quad \tilde{V}(l) = Z_L \tilde{I}(l)$$


$$\tilde{V}(l) = Z_L \tilde{I}(l) = \tilde{\Phi}_{11}[\tilde{V}_g - Z_g \tilde{I}(0)] + \tilde{\Phi}_{12} \tilde{I}(0)$$

$$\tilde{I}(l) = \tilde{\Phi}_{21}[\tilde{V}_g - Z_g \tilde{I}(0)] + \tilde{\Phi}_{22} \tilde{I}(0)$$

Then one can get:

$$\tilde{I}(0) = \frac{Z_L \tilde{\Phi}_{21} - \tilde{\Phi}_{11}}{\tilde{\Phi}_{12} - \tilde{\Phi}_{11} Z_g - Z_L \tilde{\Phi}_{22} + Z_L \tilde{\Phi}_{21} Z_g} \tilde{V}_g$$
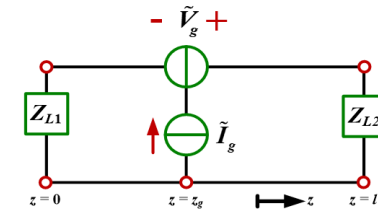
$$\tilde{I}(l) = \tilde{\Phi}_{21} \tilde{V}_g + \frac{[\tilde{\Phi}_{22} - \tilde{\Phi}_{21} Z_g][Z_L \tilde{\Phi}_{21} - \tilde{\Phi}_{11}]}{\tilde{\Phi}_{12} - \tilde{\Phi}_{11} Z_g - Z_L \tilde{\Phi}_{22} + Z_L \tilde{\Phi}_{21} Z_g} \tilde{V}_g$$




For $z < z_g$, one renames \tilde{V}, \tilde{I} as \tilde{V}_1, \tilde{I}_1

$$\begin{bmatrix} \tilde{V}_1(z) \\ \tilde{I}_1(z) \end{bmatrix} = \tilde{\Phi}(z) \begin{bmatrix} \tilde{V}_1(0) \\ \tilde{I}_1(0) \end{bmatrix} \quad \tilde{\Phi}(z) = \begin{bmatrix} \tilde{\Phi}_{11}(z) & \tilde{\Phi}_{12}(z) \\ \tilde{\Phi}_{21}(z) & \tilde{\Phi}_{22}(z) \end{bmatrix}$$

For $z > z_g$, one renames \tilde{V}, \tilde{I} as \tilde{V}_2, \tilde{I}_2
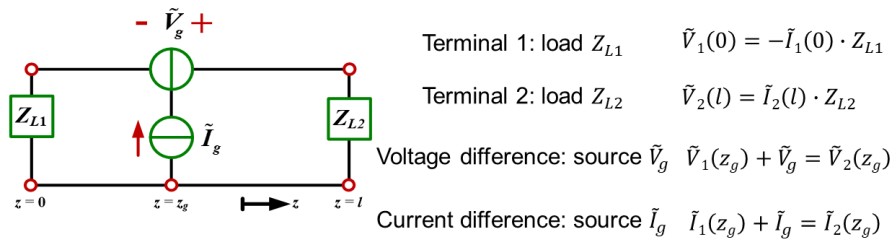
$$\begin{bmatrix} \tilde{V}_2(z) \\ \tilde{I}_2(z) \end{bmatrix} = \tilde{\Phi}(z-l) \begin{bmatrix} \tilde{V}_2(l) \\ \tilde{I}_2(l) \end{bmatrix} \quad \tilde{\Phi}(z-l) = \begin{bmatrix} \tilde{\Phi}_{11}(z-l) & \tilde{\Phi}_{12}(z-l) \\ \tilde{\Phi}_{21}(z-l) & \tilde{\Phi}_{22}(z-l) \end{bmatrix}$$





Then one can get:

$$(\tilde{\phi}_{11}(z_g) - \tilde{\phi}_{12}(z_g)/Z_{L1})\tilde{V}_1(0) + \tilde{V}_g = (\tilde{\phi}_{11}(z_g - l) + \tilde{\phi}_{12}(z_g - l)/Z_{L2})\tilde{V}_2(l)$$

$$(\tilde{\phi}_{21}(z_g) - \tilde{\phi}_{22}(z_g)/Z_{L1})\tilde{V}_1(0) + \tilde{I}_g = (\tilde{\phi}_{21}(z_g - l) + \tilde{\phi}_{22}(z_g - l)/Z_{L2})\tilde{V}_2(l)$$



For $z = l$,

$$\tilde{V}_2(l) = \frac{(1 + \Gamma_{L2})e^{-\gamma l}}{2(1 - \Gamma_{L1}\Gamma_{L2}e^{-2\gamma l})} [(e^{\gamma z_g} - \Gamma_{L1}e^{-\gamma z_g})\tilde{V}_g + (e^{\gamma z_g} + \Gamma_{L1}e^{-\gamma z_g})Z_0\tilde{I}_g]$$

$$\tilde{I}_2(l) = \frac{(1 - \Gamma_{L2})e^{-\gamma l}}{2Z_0(1 - \Gamma_{L1}\Gamma_{L2}e^{-2\gamma l})} [(e^{\gamma z_g} - \Gamma_{L1}e^{-\gamma z_g})\tilde{V}_g + (e^{\gamma z_g} + \Gamma_{L1}e^{-\gamma z_g})Z_0\tilde{I}_g]$$

For $z = 0$,

$$\tilde{V}_1(0) = \frac{(1 + \Gamma_{L1})e^{-\gamma l}}{2(1 - \Gamma_{L1}\Gamma_{L2}e^{-2\gamma l})} \{-[e^{\gamma(l-z_g)} - \Gamma_{L2}e^{-\gamma(l-z_g)}]\tilde{V}_g + [e^{\gamma(l-z_g)} + \Gamma_{L2}e^{-\gamma(l-z_g)}]Z_0\tilde{I}_g\}$$

$$\tilde{I}_1(0) = \frac{(1 - \Gamma_{L1})e^{-\gamma l}}{2Z_0(1 - \Gamma_{L1}\Gamma_{L2}e^{-2\gamma l})} \{-[e^{\gamma(l-z_g)} - \Gamma_{L2}e^{-\gamma(l-z_g)}]\tilde{V}_g + [e^{\gamma(l-z_g)} + \Gamma_{L2}e^{-\gamma(l-z_g)}]Z_0\tilde{I}_g\}$$



One can obtain $\tilde{V}(z)$, $\tilde{I}(z)$ by $\begin{bmatrix} \tilde{V}_1(z) \\ \tilde{I}_1(z) \end{bmatrix} = \tilde{\Phi}(z) \begin{bmatrix} \tilde{V}_1(0) \\ \tilde{I}_1(0) \end{bmatrix}$ $\begin{bmatrix} \tilde{V}_2(z) \\ \tilde{I}_2(z) \end{bmatrix} = \tilde{\Phi}(z - l) \begin{bmatrix} \tilde{V}_2(l) \\ \tilde{I}_2(l) \end{bmatrix}$

For $z > z_g$,

$$\tilde{V}_2(z) = \frac{e^{-\gamma z} + \Gamma_{L2}e^{\gamma(z-2l)}}{2(1 - \Gamma_{L1}\Gamma_{L2}e^{-2\gamma l})} [(e^{\gamma z_g} - \Gamma_{L1}e^{-\gamma z_g})\tilde{V}_g + (e^{\gamma z_g} + \Gamma_{L1}e^{-\gamma z_g})Z_0\tilde{I}_g]$$

$$\tilde{I}_2(z) = \frac{e^{-\gamma z} - \Gamma_{L2}e^{\gamma(z-2l)}}{2Z_0(1 - \Gamma_{L1}\Gamma_{L2}e^{-2\gamma l})} [(e^{\gamma z_g} - \Gamma_{L1}e^{-\gamma z_g})\tilde{V}_g + (e^{\gamma z_g} + \Gamma_{L1}e^{-\gamma z_g})Z_0\tilde{I}_g]$$

For $z < z_g$,


$$\tilde{V}_1(z) = \frac{e^{\gamma(z-l)} + \Gamma_{L1}e^{-\gamma(z+l)}}{2(1 - \Gamma_{L1}\Gamma_{L2}e^{-2\gamma l})} \{-[e^{\gamma(l-z_g)} - \Gamma_{L2}e^{-\gamma(l-z_g)}]\tilde{V}_g + [e^{\gamma(l-z_g)} + \Gamma_{L2}e^{-\gamma(l-z_g)}]Z_0\tilde{I}_g\}$$

$$\tilde{I}_1(z) = \frac{e^{\gamma(z-l)} - \Gamma_{L1}e^{-\gamma(z+l)}}{2Z_0(1 - \Gamma_{L1}\Gamma_{L2}e^{-2\gamma l})} \{-[e^{\gamma(l-z_g)} - \Gamma_{L2}e^{-\gamma(l-z_g)}]\tilde{V}_g + [e^{\gamma(l-z_g)} + \Gamma_{L2}e^{-\gamma(l-z_g)}]Z_0\tilde{I}_g\}$$



Product of Chain-parameter matrices

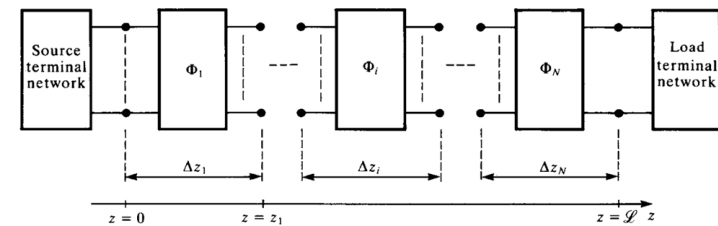The overall chain-parameter matrix of several such lines that are *cascaded* in series can be obtained as the product of the chain-parameter matrices of the sections.




$$\begin{bmatrix} \hat{V}(z_{k+1}) \\ \hat{I}(z_{k+1}) \end{bmatrix} = \hat{\Phi}_{k+1}(\Delta z_{k+1}) \begin{bmatrix} \hat{V}(z_k) \\ \hat{I}(z_k) \end{bmatrix} \quad \begin{bmatrix} \hat{V}(z_k) \\ \hat{I}(z_k) \end{bmatrix} = \hat{\Phi}_k(\Delta z_k) \begin{bmatrix} \hat{V}(z_{k-1}) \\ \hat{I}(z_{k-1}) \end{bmatrix}$$

$$\begin{aligned} \hat{\Phi}(\mathcal{L}) &= \hat{\Phi}_N(\Delta z_N) \times \cdots \times \hat{\Phi}_i(\Delta z_i) \times \cdots \times \hat{\Phi}_1(\Delta z_1) \\ &= \prod_{k=1}^N \hat{\Phi}_{N-k+1}(\Delta z_{N-k+1}) \end{aligned}$$

That's why we call "chain"!



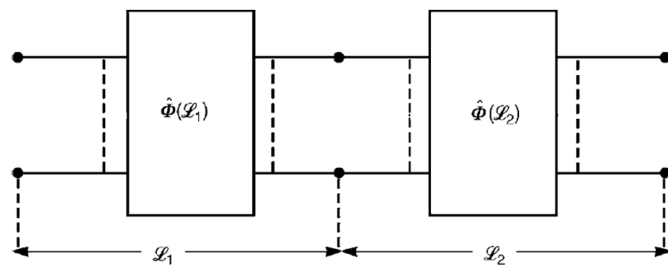

$$\hat{\Phi}(\mathcal{L}_1 + \mathcal{L}_2) = \hat{\Phi}(\mathcal{L}_2)\hat{\Phi}(\mathcal{L}_1)$$

$$\begin{aligned}\hat{\Phi}(\mathcal{L})\hat{\Phi}(-\mathcal{L}) &= \hat{\Phi}(\mathcal{L} + (-\mathcal{L})) \quad ? \\ &= \hat{\Phi}(0) \\ &= \mathbf{1}_{2n}\end{aligned}$$

quote

“History will be kind to me for I intend to write it.”

- Winston Churchill

Thank you again!